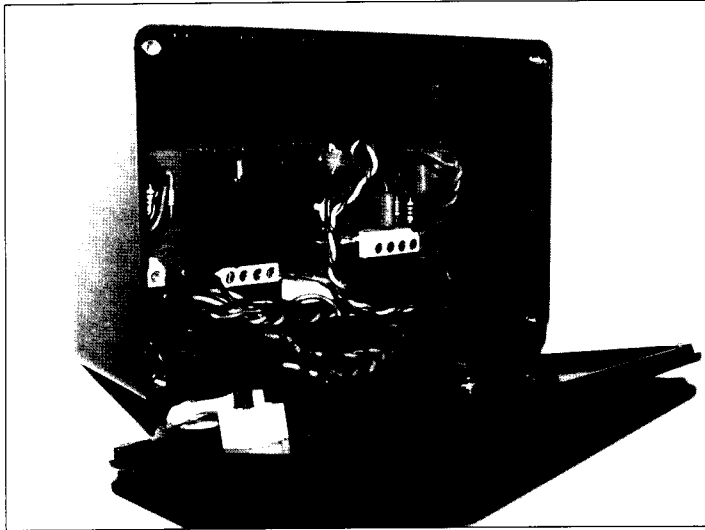


The Solar Controller



Why use a controller?

A solar water heating controller is a gadget used in conjunction with a solar water heating panel array to supply hot water to your taps. In the simplest systems, water circulates by itself. However, if you install a pump it means greater choice over where you position the panel, plus improved thermal efficiency. The controller is a simple thermostat that only switches on your pump to carry water from the heater when it's hot enough to be of use. This section tells you how to make and install one from standard electrical components.

The controller we describe can be used for most solar heated water systems. Let's look first at how it works and then at

LIST OF COMPONENTS

<u>Resistors</u>	<u>Value</u>	<u>Colour code</u>		
R1,R2	4K7 (two)	yellow, violet, red	D7	green LED (with clip)
R3,R13	100R (two)	brown, black, brown	D8	red LED (with clip)
R4,R5,R6	2K2 (three)	red, red, red	<u>Others</u>	
R7,R8	10K (two)	brown, black, orange	TR1	BC182L transistor
R9	4M7 (see note)	yellow, violet, green	IC1	LM741 op-amp
R10	1K5	brown, green, red	RLA	10A single pole changeover relay, 24V coil
R11	33OR	orange, orange, brown	T1	3 VA transformer, 240V primary, 20-0-20V secondary
R12,R14	2K2, 0.5Watt	red, red, red	S1	d.p.s.t. rocker switch, 240V AC 4A
R15	1K 1Watt	brown, black, red	S2	s.p.s.t. toggle switch, 30V DC1A
VR1	100R cermet preset		FS1	1 amp fuse
<u>Capacitors</u>				
C1	470nF capacitor polyester 100V			3 way terminal block
C2,C3	100nF capacitor polyester 100V (two)			4 way terminal block (two)
C4	330uF capacitor radial electrolytic 40V			p.c.b. terminal pins (ten)
C5	100nF suppression capacitor			fuse clips (two)
<u>Diodes</u>				plastic case
D1	8V2 zener diode			rubber grommets (three)
D2,D3,D4	1N4148 (three)			printed circuit board
D5,D6	1N4002 or 1N4007 (two)			twin 7/0.25mm cable
				epoxy putty and (maybe) silicone sealant

making the control box, fitting the sensors, choosing the temperature difference, testing procedure, installation, and some additional technical detail.

Hints on soldering

How it works

Two sensors are mounted, on the hot water tank and on the solar panel. They measure the difference in temperature between the two. When the panel is sufficiently hotter, they tell the controller automatically to switch on the pump. When the tank has heated up it will switch the pump off. There is also a manual override switch.

Building the control box

Most of the components are fitted on to a printed circuit board. This is shown in Figures 15 & 16 on the next page. Figure 14 shows the circuit diagram. The board was designed to fit inside a plastic case measuring 150mm by 80mm by 50mm, although any reasonable size may be used; you could adapt something or build it out of wood. It should be possible to solder together and construct the controller, and put it in the case, with careful reference to the diagrams and photograph. However the following points are offered to avoid some of the mistakes that might occur.

Three rubber grommets are fitted to cable holes in the lid of the case, and the LEDs and switches are fitted in the lid. Take care to position these lid-mounted parts so that there's enough clearance space when the case is put together. When fitting the diodes and the capacitor C4, make sure that their polarity is correct and that the integrated circuit IC1 is the right way round. Similarly, when completing the interwiring between the components, pay careful attention to the polarity of the LEDs, to make sure they are connected the right way round.

Check the wiring of switch S1 since this will carry mains voltage. When the components of the board are all securely soldered in place, lower the board into the case you have made and connect a three core mains cable to the three way terminal block. The cable should be fitted with a 3 amp fused plug.

Installing the sensors

First, make up the two sensor leads, one for the solar panel and one for the hot water tank. Use twin core 7/0.25mm cable. The type with one side marked with a coloured stripe or ribbing is ideal. At this stage each lead may be about 2 metres long. If necessary, extend them with more cable later; or calculate first the distance you want to position the controller from the panel and tank.

The sensors themselves are 1N4148 diodes. Simply solder them to the end of each lead as shown in Figure 17. Seal the bare wire and joints with epoxy putty against water. This will harden in a few minutes.




Thread the two sensor leads through the grommet on the end of your box and connect them into the terminal block as shown in Figure 16.

Choosing the temperature difference

The size of the temperature difference between the tank and the panel that switches the pump on or off is controlled by the component called R9. This is a feedback resistor of the 741 amplifier. You can choose its specification to give a temperature difference as shown below:

SPECIFICATION	TEMPERATURE DIFFERENCE
3M3	10°C
4M7	7°C
10M	3.5°C

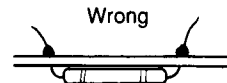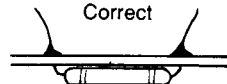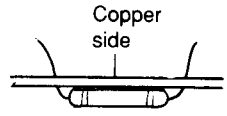
You may wish to experiment with installing different resistors at different values to find the one that works best for your conditions. Alternatively you could fit a variable resistor, and having found the optimum position, leave it there.




If you've never done any soldering before, you may find these notes useful.

- Good quality soldering is essential for good connections and proper working of the circuit.
- First push the component lead through the board, then turn the board over and slightly splay the leads to stop the component dropping out.
- Place the tip of a fine-tipped soldering iron on to the joint so that it touches both the copper board and the lead.
- After a few seconds, when it is hot, run solder on to the joint and wait until it flows completely round the lead and on to the copper track.
- Remove the iron and check that the solder has spread evenly over the joint.
- Snip the leads off with small side cutters.


Solar Water Heating - a D-I-Y Guide

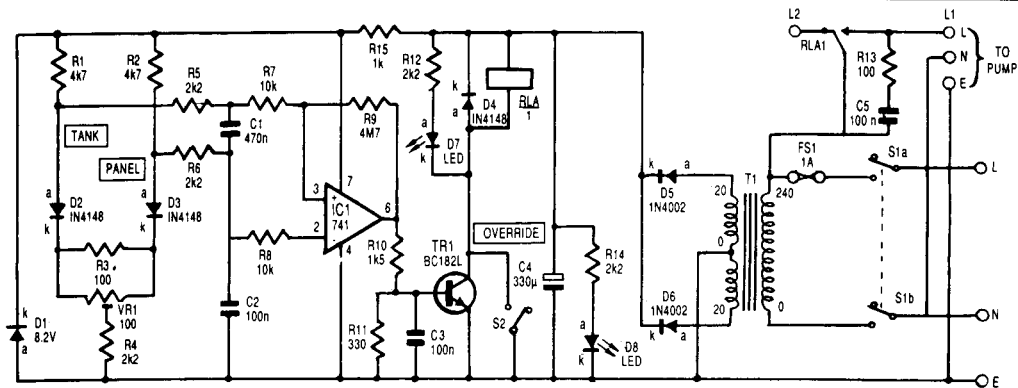


741 Connections

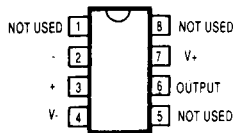

BC182L Connections

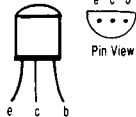

LED Connections

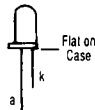


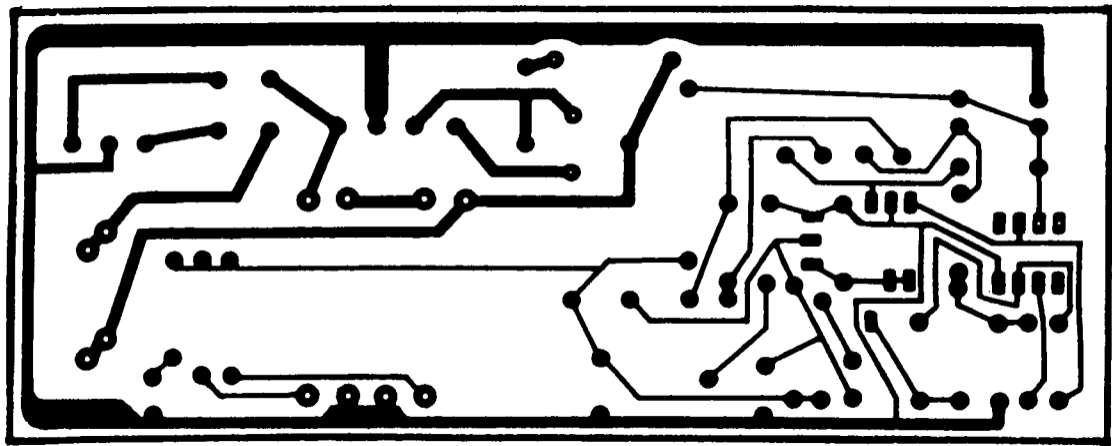


Fig. 13 (page 20):
The completed box
with the lid open
demonstrating the
circuit board and
components

Fig. 14 (top):
Complete circuit
diagram.

Fig. 15 (middle):
Full sized printed circuit
board master pattern.

Fig. 16 (below):
Component layout and
interwiring details.

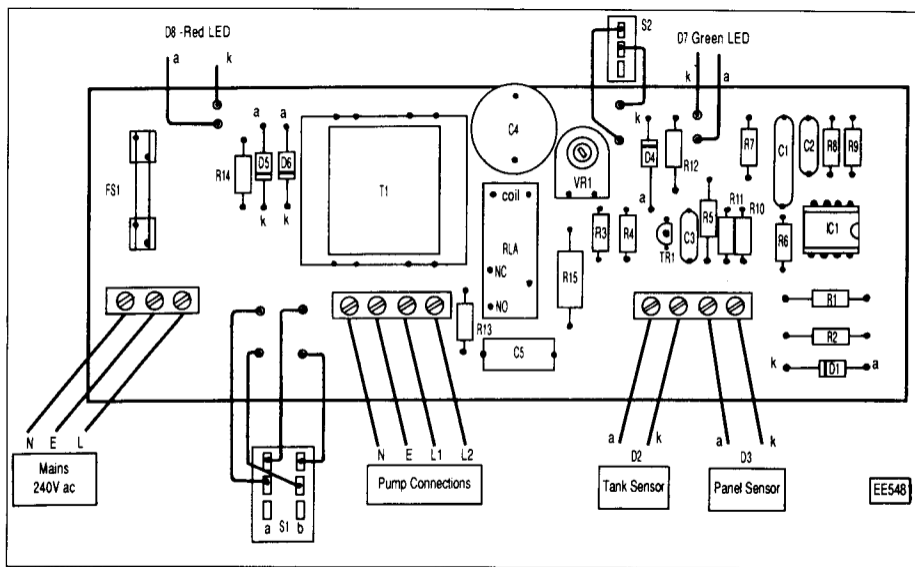

Test procedure

You're ready to try it out. Plug in the unit and turn switch S1 on. If it's all connected properly, the red LEDs should light up. Now switch S2 into the auto position. Take care. The fuse clips and components near the 3-way terminal block are now live, as is the back of switch S1.

Next, ensure that the two sensors are near to each other, and therefore at the same temperature. Turning the preset dial [VR1] should cause the relay and the green LED to turn on and off. If it does, the next step is to find the correct point at which to set VR1. This is done by turning it until the relay just comes on. Then turn it back until it is just past the point at which the relay turns off. Five degrees of rotation past the turn off point is about right. Leave it there.

You're now ready to see if a temperature difference between the sensors turns on the switch. Find something hot like a soldering iron and hold it near or against the panel sensor. The relay should click on after a few seconds. If you then leave the sensor to cool down for a few minutes the relay should turn off. If it does all this you've succeeded so far. Now disconnect the unit from the mains. You may now to install it.

Installation

Have another look at Figure 2 on page 3, which shows a typical solar heated system. The solar energy collected by the panels is pumped to the pre-heat cylinder. The pump is switched on by the solar panel controller. This pre-heated water is then drawn through the existing hot water tank.

The pump is connected to your controller on the terminals marked L1, N and E on the controller's four way terminal block. Take note of the fact that terminal L2 is live when the green LED is off.

Now you can position the controller box. It should be in a visible and accessible position so the switching of the pump can be monitored. It should also be somewhere where the temperature won't vary widely. Don't put it in the attic.

It's now time to fix the sensors. If you don't get this right, the whole system won't work. Firstly, don't run the leads near mains leads, because they cause interference. Fit the sensors in place with epoxy putty or silicone sealant and cover them with insulation, such as polystyrene. Figure 17 shows this arrangement. The tank sensor should be mounted on the pipe running from the pre-heat cylinder to the solar panels, and as near as possible to the tank. The actual connection flange is an ideal place.

The panel sensor goes on the outlet pipe inside the box of the last solar panel in the sequence. After the putty has dried, you're now ready to switch on, and the whole system should work.

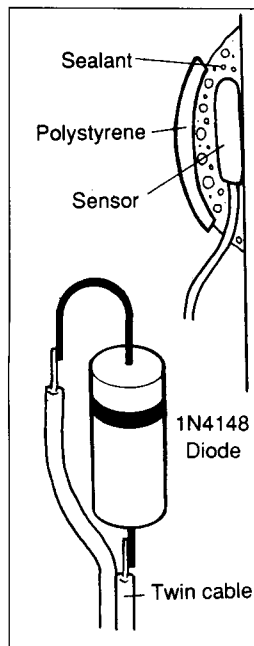


Fig. 17:
Sensor construction
and mounting

For electronics buffs

This is for electronics buffs who wish to know the functions of each of the components in the circuit.

Diodes D2 and D3 act as sensors. A current is passed through each of them via resistors R1 and R2. One property of small signal diodes is that a change of temperature will cause their forward conduction of voltage to vary in a repeatable manner. This 'differential' voltage is applied to the inputs of the IC1, which is configured to act as a Schmitt trigger with positive feedback introduced by R9.

R3 and VR1 are used to balance the Schmitt trigger inputs initially so that a differential temperature change within the desired range will be detected.

If the solar panel diode, D3, becomes hotter than the tank diode, D2, the output voltage of the amplifier will rise. Resistor R9 ensures that the output switches

cleanly between the supply rails. This turns on TR1 which activates the relay. The green LED, D7, indicates when this happens.

The power supply for the circuit comprises TR1, D5, D6 and C4, giving a full wave rectified and smoothed 30V nominal. This is then dropped through R15 and clamped by D1 at 8.2V to power the op-amp and provide a stable voltage drop across R1 and R2.

Capacitor C1 has been incorporated to reduce differential input noise. Any common mode noise is filtered by C2. C3 has been provided to reduce the effects of interference on switching transistor TR1.

C5 and R13 protect the relay contacts from the arcing that occurs when attempting to switch an inductive load. They also provide suppression of any outside electrical interference.