

Introduction to Electrical Engineering - Basic vocational knowledge (Institut für Berufliche Entwicklung, 213 p.)

➔ 6. Electrical Field

6.1. Electrical Phenomena in Non-conductors

6.2. Capacity

6.2.1. Capacity and Capacitor

6.2.2. Behaviour of a Capacitor in a Direct Current Circuit

6.2.3. Types of Capacitors

Introduction to Electrical Engineering - Basic vocational knowledge (Institut für Berufliche Entwicklung, 213 p.)

6. Electrical Field

6.1. Electrical Phenomena in Non-conductors

Electrical phenomena also occur in non-conductors. This becomes clearly evident in lightning during thunder-storms. A lightning may occur between two clouds or between cloud and earth. The cause of a lightning is a sudden charge equalisation between differently charged clouds or between different states of charge of cloud and earth. The form of discharge usually is a forked lightning. The voltage involved in lightning is about $100 \cdot 10^6$ V, the current intensity about 50 kA. With a time of discharge of 1 ms, an energy of 1000 kWh is released. Unfortunately, advantage

cannot be taken of this enormous quantity of energy. But we can protect ourselves from the dangerous effects of a lightning stroke with the help of modern technical means.

Charging with considerably lower energy takes also place due to friction between different materials, when different materials contact each other, electrons from one material can migrate to the other one. When the two materials are separated, they show different charges. Due to frequent repetition of these contacts and separations (as involved in friction), high differences in charge may occur so that discharge via a spark takes place. This phenomenon will occur only when the materials involved are extremely well insulating (in a high atmospheric humidity, many materials lose their high insulating capacity and the charges can flow off). Due to the low energy involved in the way of charging up described here, a primary danger is not given for man, but other dangers may occur due to the effects of fire or shock. Spark discharges may become dangerous when they occur in close vicinity of easily combustible liquids or explosive substances. For example, protective measures are necessary when petrol is pumped from a bulk lorry into a storage tank. To avoid spark discharge, bulk lorry and storage tank must be properly connected electrically conductive before petrol should be pumped. Force actions occur between charges. Dissimilar charges attract each other and correspondent charges repel each other (see also force actions between magnetic poles). In the printing industry this force action is disturbing. During the rapid passage of paper through the machine, the paper may be charged so that proper transport of the paper will be prevented. Similar phenomena occur in the textile industry.

Direction and intensity of the force action is described by field lines like in the magnetic field. In contrast to magnetic field lines, however, electrical field lines arise

from and end in charges. The extent of the electrical field is three-dimensional. Fig. 6.1. shows a few typical courses of field lines.

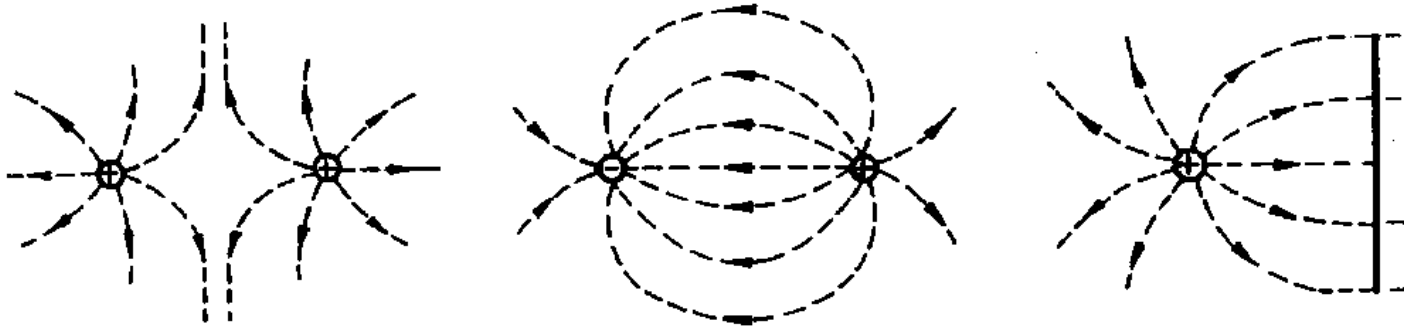


Fig. 6.1. Characteristic patterns of electric field lines

When an electrical conductor is placed in an electrical field (Fig. 6.2.), the freely movable electrons are displaced. The side facing the negative charge is positively charged and the side facing the positive charge is negatively charged. This phenomenon is called electrostatic induction or influence.

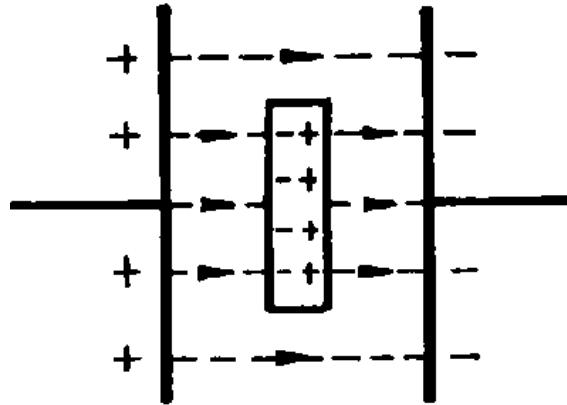


Fig. 6.2. Influence in an electric field

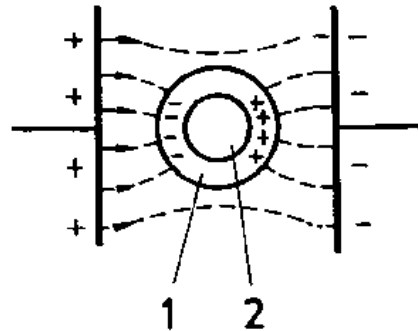


Fig. 6.3. Electrical shielding

- 1 - Metal ring**
- 2 - Field-free space**

When a conductive ring is placed in an electrical field, in the interior of the ring, a field-free space is brought about (Fig. 6.3.). This phenomenon is called electrical shielding. It is used in practice to shield from interference fields. Complicated electronic measurements are taken in Faraday's cage (working room surrounded by a double wall of copper foil) or aerial lines and other signal lines are screened.

When the electrical field acts on a non-conductor (also known as dielectric), the not freely movable electrons can be displaced only insignificantly in the direction of the positive charge. This phenomenon is called dielectric polarisation (Fig. 6.4.).

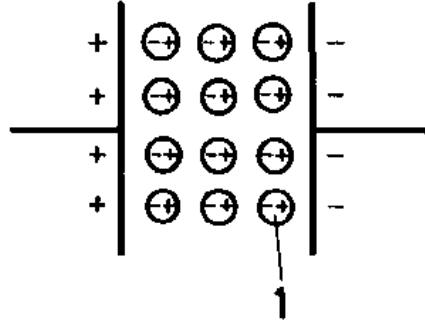


Fig. 6.4. Dielectric polarisation

1 - Elementary particle of the dielectric

If dust particles are in an electrical field, they will be charged negatively or positively, depending on their composition, attracted by the electrode having the opposite charge and deposited there. Advantage is taken of this effect in flue-gas cleaning. Dust can be removed almost completely from flue gases by means of

electrical filters. The consumption of electrical energy for 1000 m³ of flue gas to be cleaned is about 1 kWh. A voltage of about 50 kV is applied to the electrodes.

When relating the voltage between two charged plates to the distance between the latter, we obtain the field strength E.

$$E = U/l$$

$$[E] = V/m$$

(6.1.)

where:

E electrical field, strength

U voltage

l distance between the plates

This simple method of calculating the field strength is only applicable to parallel field lines (in a homogeneous field). At points and edges, the field strength is considerably higher than in the vicinity of large-area electrodes.

When the field strength reaches a critical value, the dielectric is subjected to a flashover or breakdown and, hence, to a spark discharge. The field strength required for a breakdown is called breakdown field strength. It is a quantity which depends on material (see Table 6.1.). The breakdown field strength of air is considerably lower

than that of strong insulating materials. Therefore, the distance between conductors carrying high-voltage in air must be larger than between these conductors sheathed with strong insulating materials. For example, a voltage of 330 kV can break through an distance in air of about 100 mm and through a rubber insulation of maximum 13.3 mm, however.

Table 6.1. Dielectric Strength of a Few Insulating Materials

Insulating material	Dielectric strength in kV/mm
air	3.3
paper	10
rubber	25
porcelain	15
paraffin	40
aluminium oxide	1000

Since at points and edges (small surface areas) a particularly high field strength is prevalent, flashovers preferably start from them. This phenomenon is utilised for lightning protection pointed metal rods are fastened to the highest point of buildings, the rods are connected with the ground in a properly conducting manner and so are capable of arresting lightings and carry them off to ground without any damage to the building. This point effect also entails remarkable disadvantages. Thus, charges are sparked off from lines carrying high-voltage; this leads to considerable energy losses. Therefore, it is necessary to enlarge the electrically effective surface of high-voltage lines and provide a smooth surface. An enlargement of the surface is obtained by bunch lines. The line is divided into 4 conductors which are combined

into one stranded conductor by means of spacers (Fig. 6.5.). Potential rings are attached to Insulators. Great store should be set by carefully rounded edges and smooth undamaged surfaces.

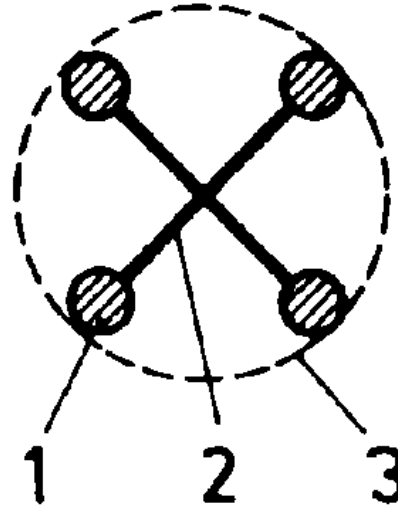


Fig. 6.5. Sectional view of a stranded conductor for highest voltage

- 1 - Individual conductor**
- 2 - Spacer**
- 3 - Electrically effective surface**

Brush discharges nevertheless occurring in extra-high voltage lines may cause luminous phenomena under certain atmospheric conditions which are called corona because of their ring shape.

Electrical phenomena also occur in non-conductors. They show different effects (lightning, spark discharge, force action). In electric filters, the force action is used for dust separation. Charges can be produced by a continuous contacting and separating (e.g. friction). Spark discharges can lead to uncontrolled actions of man due to fear, to fire and explosions. Spark discharges occur when the breakdown field strength is exceeded. Discharges primarily take place at points and edges; that is why in high-voltage engineering all conductive parts should be provided with large and smooth surfaces.

Questions and problems:

- 1. Quote examples of electrical phenomena in non-conductors!**
- 2. How are charges brought about?**
- 3. What are the facts described by the breakdown field strength?**
- 4. Why have points and edges to be avoided in high-voltage engineering?**

6.2. Capacity

6.2.1. Capacity and Capacitor

Figs. 6.2. to 6.4. show certain phenomena between two charged plates. Two plates provided with connections and separated by a dielectric are called capacitor (Fig. 6.6.). This component is capable of storing a certain charge when a certain voltage is present. This storage capability is called capacity of a capacitor.

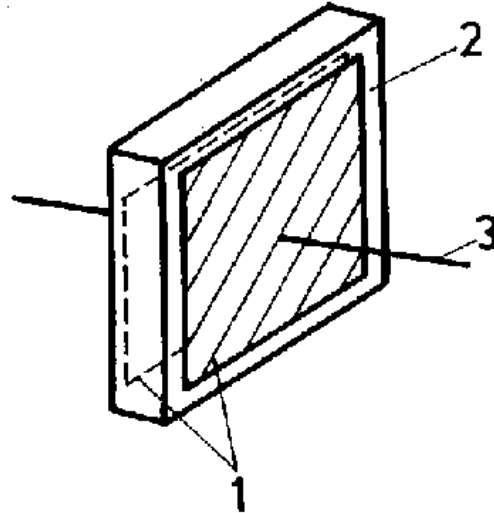


Fig. 6.6. Design of a capacitor

1 - Conducting metal plates (electrodes)

2 - dielectric

3 - Connections

$$C = Q/U$$

$$[C] = (A \cdot s) / V = F$$

(6.2.)

where:

C capacity

Q charge

U voltage

Since the unit 1 F (farad) is very great, the capacity of the capacitors manufactured only reaches fractions of 1 F. These fractions are designated by the prefixes specified by legal regulation:

$$1 \text{ pF} = 1 \text{ picofarad} = 10^{-12} \text{ F}$$

$$1 \text{ nF} = 1 \text{ nanofarad} = 10^{-9} \text{ F}$$

$$1 \text{ }\mu\text{F} = 1 \text{ microfarad} = 10^{-6} \text{ F}$$

The storage capacity of a capacitor is dependent on the area of the electrodes, the distance between them and the type of dielectric.

$$C = \epsilon A/d$$

(6.3.)**where:**

ϵ 1) dielectric constant

A area of the electrodes

d distance between the electrodes

1) ϵ Greek letter epsilon

The material constant is usually stated for the dielectric in question in the form of the product of the absolute dielectric constant times the relative dielectric constant.

$$\epsilon = \epsilon_0 \cdot \epsilon_r$$

(6.4.)

where:

ϵ_0 absolute dielectric constant

ϵ_r relative dielectric constant

The absolute dielectric constant applies to vacuum and is

$$\epsilon_0 = 8.86 \cdot 10^{-12} \text{ (A} \cdot \text{s)/(V} \cdot \text{m)}$$

Table 6.2. ϵ_r of Some Insulating Materials

Insulating material	ϵ_r
air	1
paper	2

transformer oil	2.5
rubber	2.7
porcelain	5
Epsilon (special ceramic compound for the production of capacitors)	up to 10,000

Like resistors, capacitors can be connected in series or in parallel. The total capacity obtained in this way is to be determined. Fig. 6.7. shows the series connection of two capacitors. The two capacitors have the same charge Q . The following holds:

$$Q_{AB} = Q_1 = Q_2$$

$$U_{AB} = U_1 + U_2$$

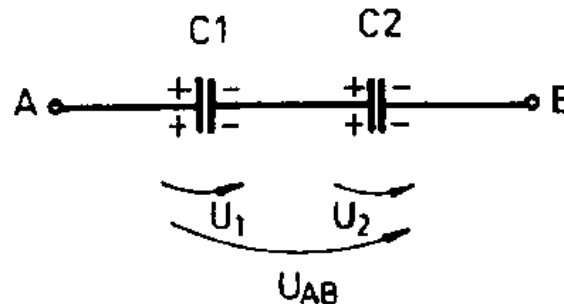


Fig. 6.7. Capacitors connected in series

When dividing the voltage equation by the charge, we have

$$U_{AB}/Q = U_1/Q + U_2/Q$$

After inversion, we obtain from equation 6.2.

$$1/C = U/Q$$

and, for the total capacity of a series connection of capacitors we have

$$1/C_{\text{equ}} = 1/C_1 + 1/C_2$$

(6.5.)

This equation has the same structure as the equation for the determination of R_{equ} of a parallel connection of resistors.

The parallel connection of two capacitors is shown in Fig. 6.8. The same voltage is applied to the two capacitors, and each capacitor has stored a charge in accordance with its capacity.

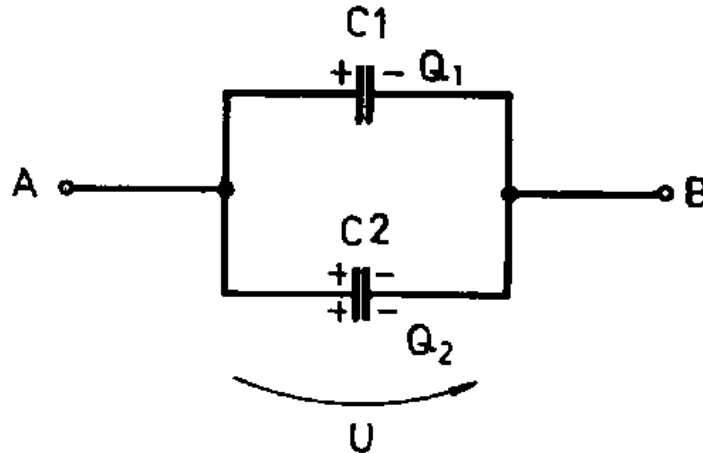


Fig. 6.8. Capacitors connected in parallel

Thus, we have

$$U = U_{C1} = U_{C2}$$

$$Q_{AB} = Q_1 + Q_2$$

After division, we obtain

$$Q_{AB}/U = Q_1/U + Q_2/U$$

and with equation 6.2. we have

$$C_{equ} = C_1 + C_2$$

(6.6.)

This equation has the same structure as the equation for the determination of R_{equ} of a series connection of resistors.

From the equations 6.5. and 6.6., the following general statement can be derived: In a series connection of capacitors, the total capacity is always smaller than the smallest individual capacity, and in a parallel connection of capacitors, the total capacity is always greater than the greatest individual capacity.

Example 6.1.

Two capacitors with a capacity of 470 nF and of 680 nF have to be connected in series and then in parallel. Determine the total capacity of each of the two types of connections!

Given:

$$C_1 = 470 \text{ nF}$$

To be found:

C in series connection and in parallel connection

Solution:

Series connection of C_1 and C_2

$$1/C_{\text{equ}} = 1/C_1 + 1/C_2 = (C_2 + C_1)/(C_1 \cdot C_2)$$

$$C_{\text{equ}} = (C_1 \cdot C_2)/(C_1 + C_2)$$

$$C_{\text{equ}} = (470 \text{ nF} \cdot 680 \text{ nF})/(470 \text{ nF} + 680 \text{ nF})$$

$$\underline{C_{\text{equ}} = 277.9 \text{ nF}}$$

Parallel connection of C1 and C2

$$C_{\text{equ}} = C_1 + C_2$$

$$C_{\text{equ}} = 470 \text{ nF} + 680 \text{ nF}$$

$$C_{\text{equ}} = 1150 \text{ nF}$$

$$\underline{C_{\text{equ}} = 1/15 \mu\text{F}}$$

In series connection, a total capacity of 277.9 nF is obtained while in parallel connection the total capacity is 1.15/μF.

6.2.2. Behaviour of a Capacitor in a Direct Current Circuit

An uncharged capacitor is connected to a direct voltage source according to Fig. 6.9. (switch position 1).

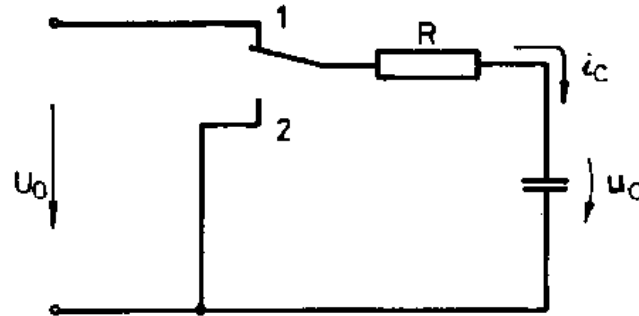


Fig. 6.9. Circuit for charging and discharging a capacitor

The terminal voltage of the uncharged capacitor is 0. In order that, between the plates of the capacitor, the voltage can be applied to which it is connected, the capacitor must be charged. This means that a charging current must flow at the instant of switching on. The intensity of the current at the instant of switching on is determined by the large difference between charging voltage and terminal voltage of the capacitor and the resistance. With increasing charge of the capacitor, the voltage of it increases and will reach the value of the charging voltage when the process of charging is finished. With increasing charge, the voltage difference between charging voltage and terminal voltage of the capacitor also drops and, consequently, the charging current also drops. At the end of charging, the voltage difference and the charging current are 0. A direct current is no longer allowed to flow now. This is also due to the design of the capacitor because a dielectric (insulating material) is between its two connections.

When the capacitor is now discharged via a resistor according to Fig. 6.9. (switch position 2), at the first instant of discharge, a discharge current must flow which is

only limited by the resistance. Since, due to the discharge, the terminal voltage of the capacitor drops, the discharge current must also drop in the course of time. After complete discharge, the terminal voltage and the discharge current have dropped to 0. The course taken by current and voltage during charging and discharging is shown in Fig. 6.10. Charging commences at time t_1 and discharging at time t_2 . It is evident that charging and discharging currents suddenly reach their maximum value at the beginning of the charging or discharging process and then they reach the value of 0 after some time. Both in charging and in discharging, the voltage changes its value only slowly. There are no sudden voltage changes in capacitors.

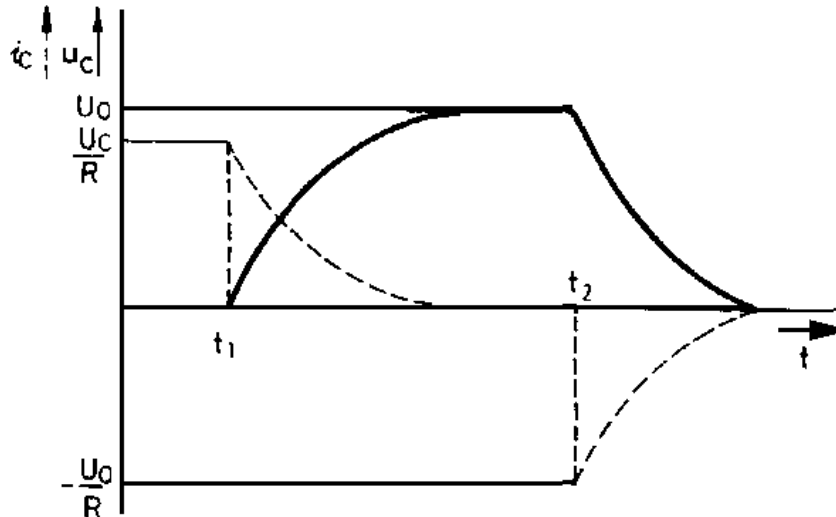


Fig. 6.10. Behaviour of current and voltage during the charging and discharging of a capacitor $t_{\text{ein}} = t_{\text{on}} \cdot t_{\text{aus}} = t_{\text{off}}$

Since the peak value of the discharge current is limited only by the discharge resistance, a capacitor should not be discharged via a short circuit. If this would occur, however, at the first instant of discharge, an extremely high current would flow for a short time which might cause the destruction of the capacitor or a fusing of the shorting bridge. As a capacitor retains its charge for some time after charging without external discharge, particular caution is necessary when working at installations containing capacitors. After disconnection from the mains, the fact that the capacitors are completely discharged must be checked or discharge via a resistor must be effected. In many installations, a discharge resistance is incorporated in order to avoid dangers to man.

During discharging, a capacitor acts as an electrical energy source (during a certain time, its terminal voltage drives a current). The energy stored in a capacitor is written as

$$W = C/2 \cdot U^2$$

(6.7.)

where:

W energy

C capacity

U voltage

The energy that can be stored in a capacitor is relatively small. It is of advantage

however, that it is available as a short-time energy release. Advantage of this effect is taken in a photoflash device and in some spot-welding equipment.

Example 6.2.

Which energy is stored in a capacitor of 47 μF charged up to 100 V?

Given:

$$U = 100 \text{ V}$$

$$C = 47 \mu\text{F}$$

To be found:

$$W$$

Solution:

$$W = C/2 \cdot U^2$$

$$W = 23.5 \cdot 10^{-6} (\text{A} \cdot \text{s})/\text{V} \cdot 10^4 \text{ V}^2$$

$$W = 0.235 \text{ Ws}$$

$$\underline{W = 235 \text{ mWs}}$$

The energy stored in the capacitor is 235 mWs.

6.2.3. Types of Capacitors

For the different fields of application, a great variety of designs of capacitors is

available. In heavy current engineering, primarily paper capacitors in a metal cup are used (Fig. 6.11.). Two metal foils and two paper strips are placed one upon the other in the way shown in the illustration and then properly rolled up. The two metal foils are attached to connections and the roll is mounted in a metal cup. Such a paper capacitor is also known as roll-type capacitor. The MP-capacitor (metal-paper capacitor) is designed in a similar manner; in this case, the foil is replaced by a coat of metal which is produced by vapour deposition. These capacitors are smaller than paper capacitors of the same capacity.

Fig. 6.11. Encased capacitor

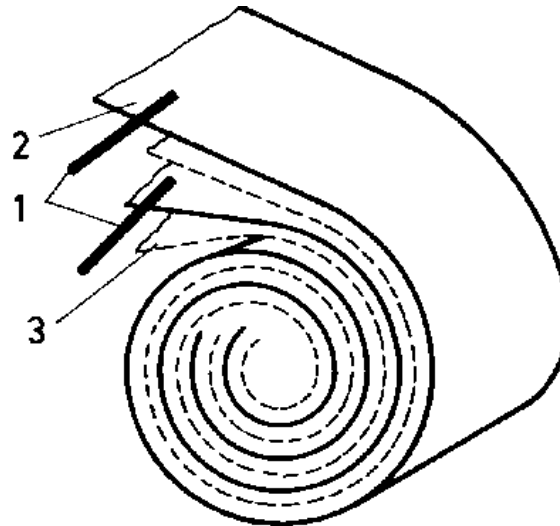


Fig. 6.11.a Design of the roll

- 1 - Connections of the foils**
- 2 - Metal foil**
- 3 - Paper strips**

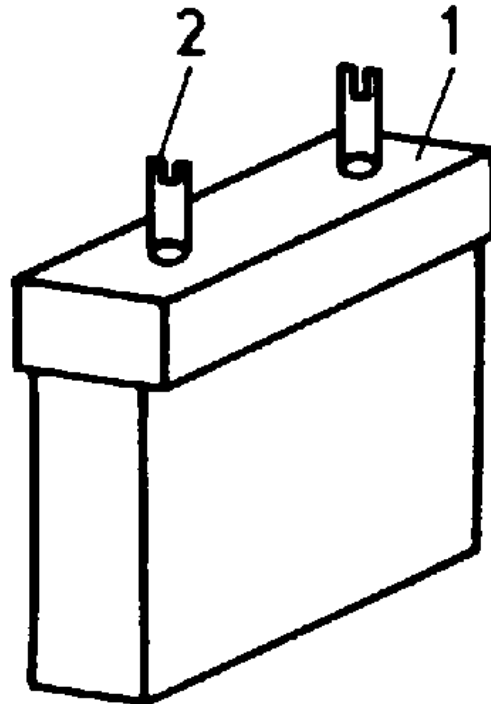


Fig. 6.11.b External view of the capacitor

- 1 - Metal enclosure**

2 - Connections

Another advantage of MP-capacitors is the fact that, after a breakdown or puncture of the dielectric, the extremely thin metal coat in the close vicinity of the puncture evaporates and, thus, removing the short-circuit - that is why MP-capacitors are called "self-healing" capacitors.

For the practical use, the value of the capacity printed on the device and the rated voltage up to which the capacitor may be used have to be observed.

An arrangement consisting of two plates with a dielectric between them is called capacitor. The capacity of a capacitor is a measure of the charge which the capacitor is capable of storing at a certain voltage, and it is also dependent on the design. The total capacity in series connection and in parallel connection of capacitors is expressed by the equations 6.5. and 6.6.

When a capacitor is connected to a direct voltage, a current will only flow during charging and discharging. There are not sudden voltage changes in a capacitor. A charged capacitor can retain its charge for a longer period of time (danger!) and it should never be discharged via a short circuit. The capacitor may be used as an energy store.


In heavy current engineering, the paper capacitor arranged in a metal cup is used. For use, pay particular attention to the value of the capacity and the rated voltage.

Questions and problems:

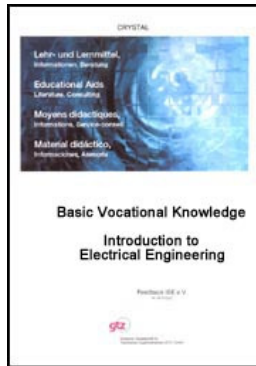- 1. Describe the basic design of a capacitor and, in particular, the design of a paper capacitor!**
- 2. Which property of the capacitor is described by the capacity?**
- 3. Explain the course taken by current and voltage during charging and discharging of the capacitor!**
- 4. Why should capacitors not be discharged via a short circuit?**
- 5. What should be strictly observed when working at installations incorporating capacitors?**







[Home](#) > [ar.cn.de.en.es.fr.id.it.ph.po.ru.sw](#)



Introduction to Electrical Engineering - Basic vocational knowledge (Institut für Berufliche Entwicklung, 213 p.)

7. Alternating Current

-  7.1. Importance and Advantages of Alternating Current
-  7.2. Characteristics of Alternating Current
-  7.3. Resistances in an Alternating Current Circuit
-  7.4. Power of Alternating Current

Introduction to Electrical Engineering - Basic vocational knowledge (Institut für Berufliche Entwicklung, 213 p.)

7. Alternating Current

7.1. Importance and Advantages of Alternating Current

In the preceding Sections, we have explained the electro-technical conformities with natural laws under the restricting condition that current intensity and magnitude of voltage remain constant with respect to time. In practice, however, especially in power electrical engineering, mainly alternating current is used.

Alternating current is a current whose magnitude and direction varies periodically; this also applies to alternating voltage.

The electrical laws naturally also apply to alternating current engineering; a few peculiarities have to be observed, however.

Of the various possible forms, the sinusoidal alternating current has the greatest importance. Its substantial advantages are as follows:

- **simple and economical generation**
- **transformation into other values (principle of mutual induction)**
- **low-loss energy-transmission even through large distances**
- **the sinusoidal form is not changed by the basic components R, L and C**

Because of these and other advantages, alternating current engineering is of paramount importance. If direct current is required (e.g. for the operation of the

majority of electronic devices), it can easily be produced by rectifying the alternating current. In practice, especially in power electrical engineering, alternating current is used because of many advantages. This is a current whose magnitude and direction varies periodically. The sinusoidal alternating current has the greatest importance.

7.2. Characteristics of Alternating Current


Alternating current and alternating voltage are produced in generators. In Section 5.3.2. the generator principle has been pointed out. Below, explanations in great detail are given.

When turning a coil (represented by a conductor loop in Fig. 7.1.) in a magnetic field, a voltage which can drive a current is induced in this coil. The direction can be determined with the help of the right-hand rule. At a constant rotational speed, magnitude and direction of the induced voltage is dependent on the position of the conductor loop.

Fig. 7.1. Model of an alternating current generator


1 - North pole

2 - South pole

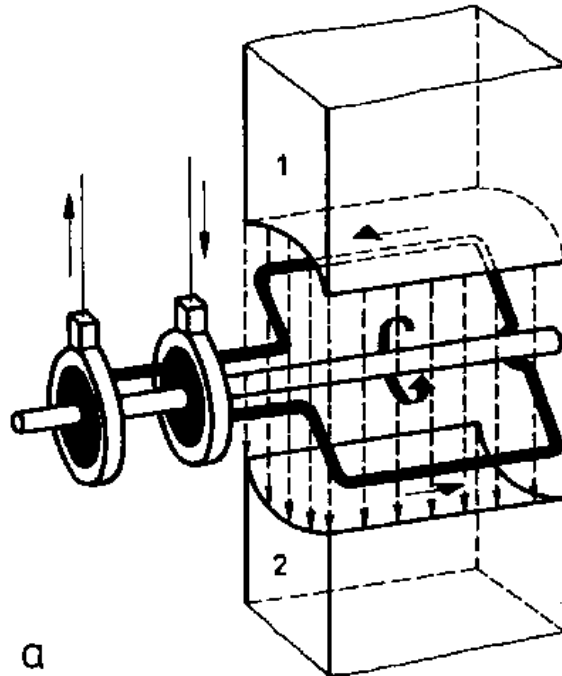

a

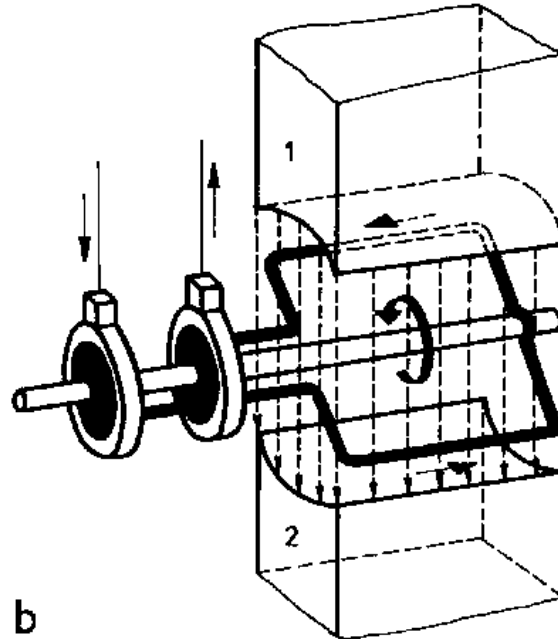a) Position of the loop of conductor at a certain instant



b) Position of the loop of conductor after half a revolution

In horizontal position, the entire magnetic flux penetrates the loop, $\Delta\Phi/\Delta t$ has the smallest value and the induced voltage is equal to zero. In vertical position, (parallel to the magnetic fields), the rate of flux variation $\Delta\Phi/\Delta t$ is maximum and the induced voltage has the highest value. Upon further rotation, the voltage again drops and after half a revolution reaches the value of zero. In the further course, the voltage changes its direction and reaches its negative maximum value in vertical position. After one full revolution, the initial condition is again reached, the voltage has

dropped to zero and another cycle with exactly the same course can begin. In Fig. 7.2., the described conditions are shown for eight selected positions of the conductor. The behaviour of the curve is a sine function.

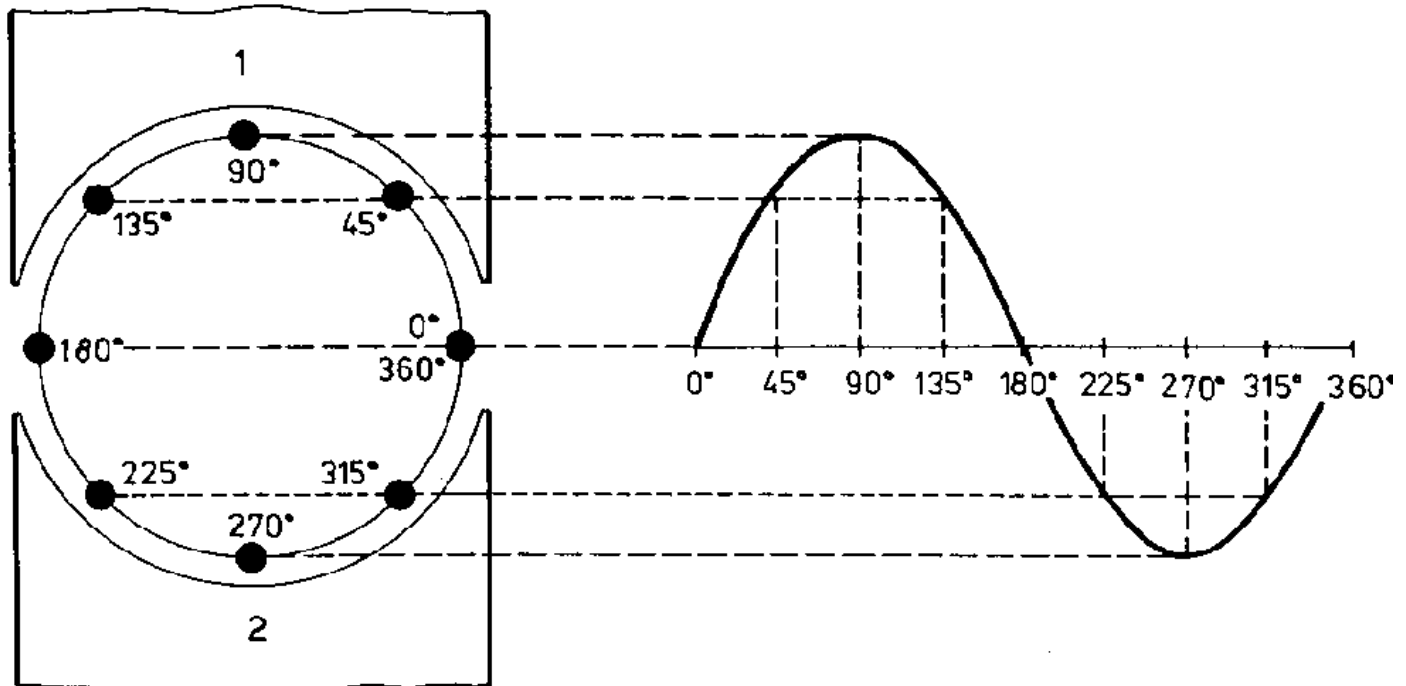


Fig. 7.2. Development of a sinusoidal voltage or current curve

1 - North pole

2 - South pole

Frequently, the angle is expressed in circular measure; the correlation is easily given with the circumference of a circle having the radius $r = 1$. We have:

Circumference of a circle $C = 2 r\pi = 2\pi$; the perigon of a circle is $\alpha = 360^\circ$; this means

that $360^\circ \hat{=} 2\pi$ and, hence, $180^\circ \hat{=} \pi$, $90^\circ \hat{=} \frac{\pi}{2}$, $45^\circ \hat{=} \frac{\pi}{4}$ etc.

The voltage and current course represented in Fig. 7.2. is called oscillation, cycle or wave. Each wave is made up of a positive (1) and a negative (2) half wave. The time for a full revolution of the conductor loop is called time of oscillation or duration of a cycle (formula sign T). The angular velocity at which the conductor loop rotates is the angle through which the loop has passed in a certain unit of time. With a perigon of $360^\circ = 2\pi$, the duration of a cycle T is required. The angular velocity ω is usually called angular frequency ω ¹⁾ in electrical engineering and it is written as

1) ω Greek letter omega

$$\omega = 2\pi/T$$

(7.1.)

where:

ω angular frequency

T duration of a cycle

2π circular measure of the circle (= circumference of the unit circle)

The product of ωt is the angle α at time t and at the angular frequency ω ; $\alpha = \omega t$. This angle is called phase angle or, in short, phase. The phase is the condition of oscillation given at a certain time which is repeated at the same time intervals.

When, for example, $t = T/4$, then $\alpha = \omega \cdot T/4$. Using $\omega = 2\pi/T$ from equation (7.1), we

have $\alpha = 2\pi/T \cdot \frac{T}{4} \triangleq \frac{\pi}{2} = 90^\circ$. This is the phase angle at a quarter of a cycle. The number of cycles or waves produced in a certain time (e.g. $t = 1$ s) is called frequency f of the alternating voltage or alternating current. The greater the duration of a cycle T , the smaller the frequency f . Fig. 7.3. shows two different curves for a duration of 1 s. The curve drawn as a solid line is a cycle, its duration $T = 1$ s. The curve represented by a dashed line covers five cycles (the frequency is higher), and the duration of a cycle $T = 1/5$ s = 0.2 s

$$f = 1/T$$

(7.2.)

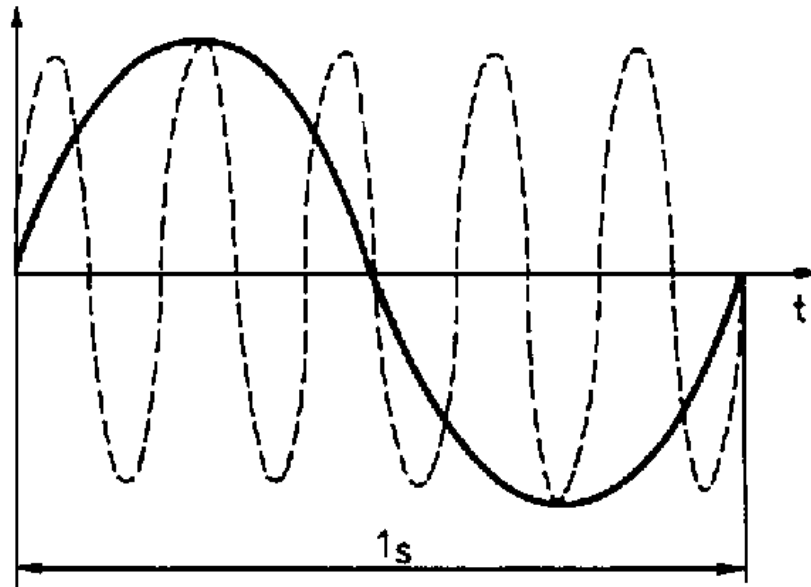


Fig.7.3 Alternating currents with frequencies of 1 Hz and 5 Hz

where:

f frequency

T duration of a cycle

In honour of the German physicist Heinrich Hertz (1857 - 1894), the unit of frequency is called Hertz = Hz.

The following subunits are frequently required

1 kHz = 1 kilohertz = 10^3 Hz

1 MHz = 1 megahertz = 10^6 Hz

1 GHz = 1 gigahertz = 10^9 Hz

The correlation between the angular frequency and frequency is given by the equations (7.1.) and (7.2.).

$$\omega = 2\pi f$$

(7.3.)

Another rarely used characteristic for the electrical wave is the wavelength λ ¹⁾. Wavelength is the length of a wave measured in a unit of length (e.g. m, km, cm, mm). As the electrical energy propagates with light velocity

1) λ Greek letter lambda

$$c = 300,000 \text{ km/s}$$

the distance over which a wave extends can be calculated on the basis of a given frequency. We have:

$$c = \lambda f;$$

after inversion we obtain for the wavelength

$$\lambda = c/f$$

(7.4)**where:** λ wavelengthc velocity of propagation ($c = 300,000 \text{ km/s} = 3 \cdot 10^8 \text{ m/s}$)

f frequency

$$[\lambda] = \text{m/s} \cdot 1/\text{s} = \text{m}$$

The magnitude of the alternating voltage or the alternating current can be determined on the basis of the sine curve developed in Fig. 7.2. The maximum value occurring at 90° and 270° is called peak value, maximum value or amplitude and is designated by (or). All other values which vary continuously and, thus, are different at any time are called instantaneous values and are designated by u (or i).

When the maximum value is known the instantaneous values can be determined at any time. The general equation of a sinusoidal alternating current is

$$u = \sin \omega t$$

(7.5.)**where:**

u instantaneous value
maximum value, peak value or amplitude
 $\sin \omega t$ factor of the sine function at angle

Besides an exclusively mathematical treatment, alternating current processes are frequently represented in diagrams which offer a better survey. Particularly suitable for this purpose are vector and line diagrams.

Vector diagram

The alternating voltage or the alternating current is represented by a pointer (vector) capable of rotating whose length corresponds to the peak value. This pointer rotates anticlockwise at the angular velocity ω . The pointer position at any time indicates the position of the conductor loop. In order to determine the instantaneous value of voltage or current for any desired position, a straight line is drawn from the pointer tip to the horizontal axis which passes through the centre of the circle. The length of the straight line corresponds to the instantaneous value in question (Fig. 7.4.a). The particular advantage of the vector diagram is lucidity; a disadvantage is the fact that the conditions can be represented only for one point of time or for a few selected instants.

Line diagram

The alternating voltage or alternating current is represented by a sine curve from which the values for all instants can be read off (Fig. 7.4.b). The line diagram can be developed from the vector diagram in the following manner. Close by the vector diagram, a horizontal line is drawn. This line is divided into periods, the smallest one

being equal to the duration of one cycle T , or into angular degrees up to $360^\circ \cong 2\pi$. Perpendicular lines are drawn from the points of division which resemble the lines on the vector diagram as to size and direction, when connecting the end points of the perpendicular lines, the sine curve is obtained. Fig. 7.4. shows the construction described. For reasons of clearness, the vector diagram (Fig. 7.4.a) only shows the vectors for 30° , 60° , 90° , 180° and 225° . The advantage of the line diagram is the possibility of representing all of the instantaneous values; a disadvantage is the restricted lucidity especially when several curves have to be represented.

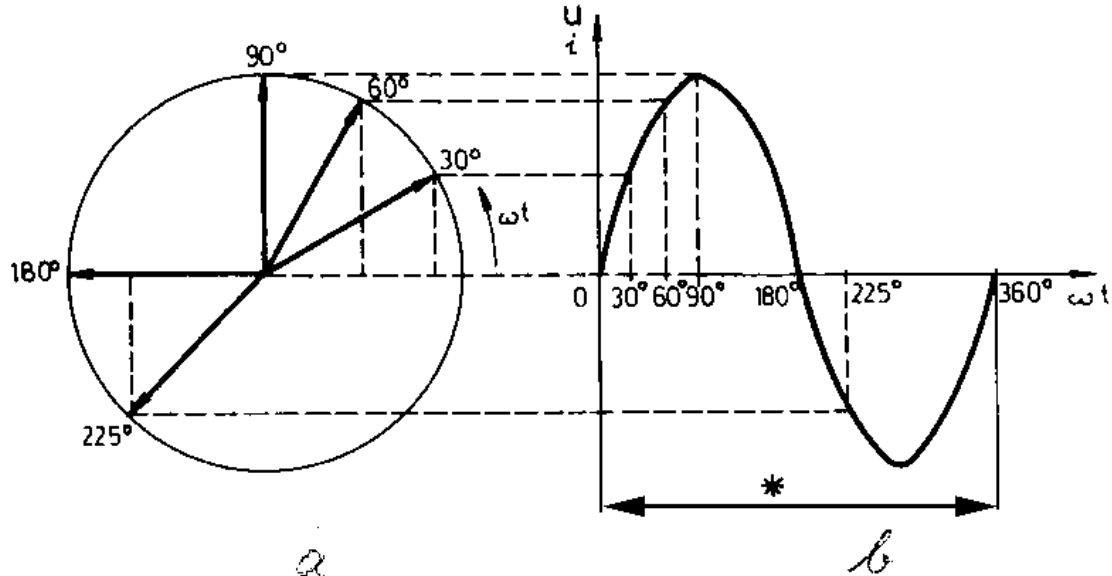


Fig. 7.4. Graphical representation, of the alternating current and alternating voltage

- a) **Vector diagram**
- b) **Line diagram**

1 Periode = 1 cycle

Example 7.1.

A sinusoidal alternating voltage having a frequency of $f = 50$ Hz has a peak value = 311 V. Draw the vector diagram for the angles of rotation $\omega t = 30^\circ, 45^\circ, 60^\circ$ and develop the line diagram on this basis! Further, determine the angular frequency, the duration of a cycle T , and the wavelength λ !

Given:

$$= 311 \text{ V}$$

$$f = 50 \text{ Hz}$$

$$\omega t = 30^\circ, 45^\circ, 60^\circ$$

To be found:

vector and line diagrams

ω

T

λ

Solution: (Fig. 7.5.)

$$\omega = 2 f$$

$$\omega = 2 \cdot 3.14 \cdot 3.14 \cdot 50 \text{ 1/s}$$

$$\omega = \underline{\mathbf{314 \text{ 1/s}}}$$

$$\mathbf{T = 1/f}$$

$$\mathbf{T = 1/50 \text{ s} = 0.02 \text{ s}}$$

$$\mathbf{T = 20 \text{ ms}}$$

$$\lambda = c/f$$

$$\lambda = \frac{3 \cdot 10^8 \text{ m/s}}{50 \cdot 1/\text{s}} = 6 \cdot 10^6 = 6,000 \cdot 10^3 \text{ m}$$

$$\lambda = \mathbf{6,000 \text{ km}}$$

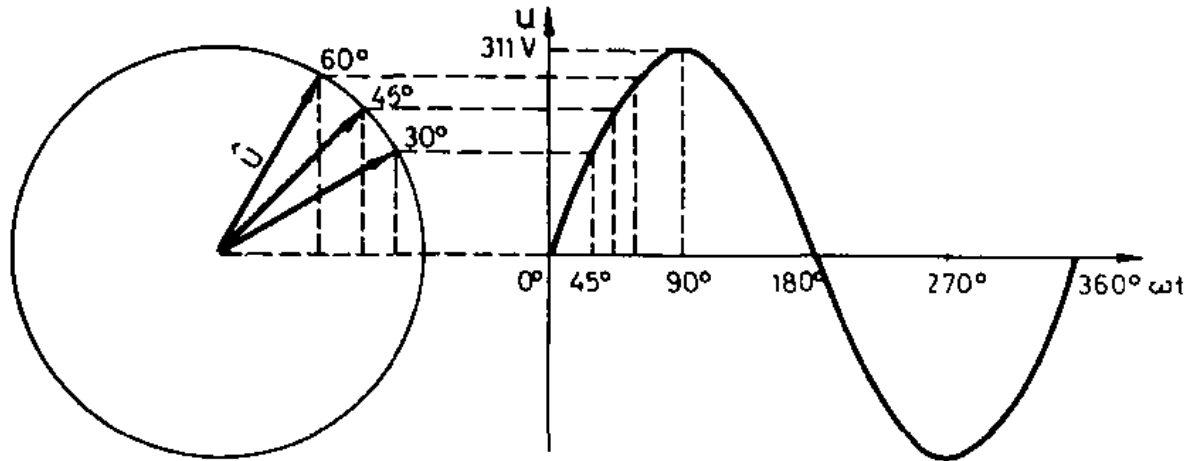


Fig. 7.5. Vector diagram and line diagram for example 7.1.

Like direct current, alternating current lends itself to the operation of heating and thermal appliances as well as incandescent lamps. Alternating current motors are used for the conversion into mechanical energy. Since alternating current, in contrast to direct current, continuously changes its magnitude and direction, a mean value must be found which has the same effect as a corresponding direct current. This mean value is called effective value (or root mean square value = r.m.s. value).

In Section 4.1., the energy conversion and the power of the current have been represented in general and the relation $P = I^2 R t = U^2 / R \cdot t$ has been derived. Evidently, it is the square of the current intensity and of the voltage that matters. In case of alternating current, we have to square all instantaneous values. Of all squared values of a cycle, the arithmetic mean must be formed. In this way, the square of the effective value is obtained. This is illustrated by Fig. 7.6. The sine curve has been squared.

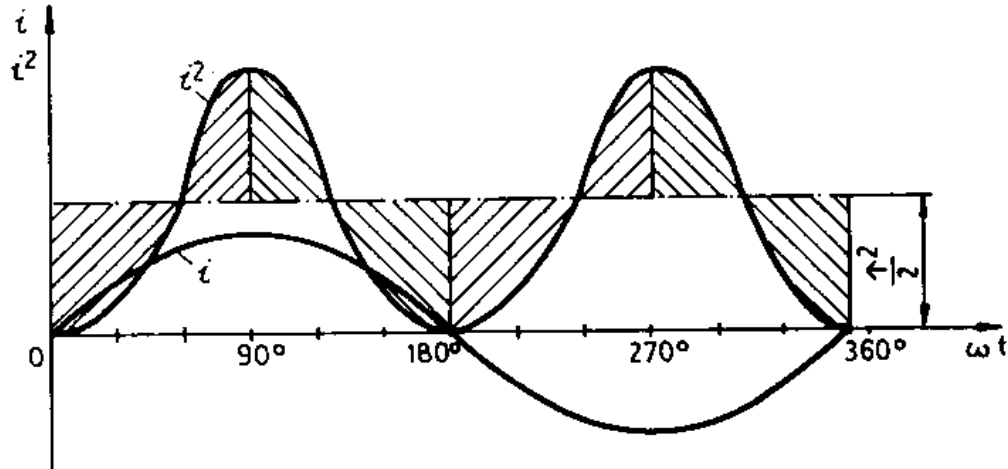


Fig. 7.6. Determination of the effective value of the alternating current

In this way, all values, even those of the negative half wave, become positive. The squared sine curve is also sinusoidal but has double the frequency of the original curve. The arithmetic mean is $I^2/2$.

This value is the square of the effective value I , hence,

$$I^2 = \frac{I_m^2}{2}; \text{ and, with respect to voltage, } V^2 = \frac{V_m^2}{2}$$

By extraction of roots in the equation, we obtain

$$I = \frac{\hat{I}}{\sqrt{2}} \text{ or } U = \frac{\hat{U}}{\sqrt{2}}$$

Since $\sqrt{2} = 1.414$ and $1/\sqrt{2} = 0.707$, we obtain for the current

$$I = 0.707 \text{ or } = 1.414 I$$

(7.6.a)

and for the voltage

$$U = 0.707 \text{ or } = 1.414 U$$

(7.6.b)

A sinusoidal alternating current causes the same thermal effect as a direct current of intensity I if its peak value I is 1.414 times the current intensity of the direct current. Analogous conditions hold for the sinusoidal alternating voltage.

Example 7.2.

Two usual mains voltages have the following values:

a) $U = 220 \text{ V}$;

b) $= 535 \text{ V}$. Determine the peak voltage for a) and the r.m.s. voltage for b)

Given:

a) $U = 220 \text{ V}$

b) $U = 535 \text{ V}$

To be found:

a)

b) U

$$\begin{aligned} \text{Solution: a) } &= 1.414 U & \text{b) } &U = 0.707 \\ &= 1.414 U \cdot 220 \text{ V} & &U = 0.707 \cdot 535 \text{ V} \\ &= \underline{311 \text{ V}} & &\underline{U = 380 \text{ V}} \end{aligned}$$

In the general use of alternating voltages and alternating currents, always effective (r.m.s.) values are involved.

When turning a coil in a magnetic field, a voltage is induced in the coil which changes periodically with respect to magnitude and direction. The voltage and current path produced during one revolution is called oscillation, cycle or wave. The most important characteristics of a wave are duration of a cycle, frequency, angular frequency, wavelength, phase, instantaneous value, peak value or maximum value or amplitude. Any sinusoidal quantity can be described mathematically, namely, analytically by an equation, graphically by a vector diagram or a line diagram.

The value of an alternating quantity (voltage or current) is called effective

value (or r.m.s. value) if the same thermal effect is produced as caused by a corresponding direct quantity (voltage or current). Current and voltage data without special designation are always effective values in alternating current engineering.

Questions and problems:

1. Determine the duration of a cycle, angular frequency, and wavelength of the oscillations with the following frequencies

- a) technical alternating current $f = 50 \text{ Hz}$
- b) test tone for electrical paths $f = 16 \cdot 2/3 \text{ Hz}$
- c) test tone for telecommunication installations $f = 1 \text{ kHz}$
- d) transmitter frequency of a long-wave transmitter $f = 182 \text{ kHz}$
- e) transmitter frequency of a short-wave transmitter $f = 6115 \text{ kHz}$
- f) transmitter frequency of a VHF transmitter $f = 97.15 \text{ MHz}$

2. What are the advantages and disadvantages of the vector diagram as compared, with the line diagram?

3. Draw the vector and line diagrams of an alternating voltage whose frequency is 50 Hz, peak value 156 V and zero-phase angle 30°! Select a suitable scale!

4. Determine the peak values of the following sinusoidal quantities:

a) 6 V

- b) 380 V**
- c) 15 kV**
- d) 200 μ A**
- e) 10 A**
- f) 25 A**

5. The peak values of the following sinusoidal quantities are given s

- a) 311 V**
- b) 70.7 mV**
- c) 8.5 A**
- d) 4.25 mA**

Find the effective values!

7.3. Resistances in an Alternating Current Circuit

Effective resistance R

Loads which completely convert the electrical energy into heat energy are called effective resistances. They include thermal appliances, incandescent lamps and wire and film resistors used for current limitation. The behaviour of effective resistances in alternating current is the same as in direct current. Ohm's law dealt with in Section 3.2. is applicable to them without any restriction. Its resistance value R is independent of the frequency of the alternating current (Fig. 7.7.). The voltage has the same phase as the current. In Fig. 7.8., the vector diagram and the line diagram for current and voltage with an effective resistance is represented. Ideal effective resistances, also known as active resistances, have no inductance and no capacity.

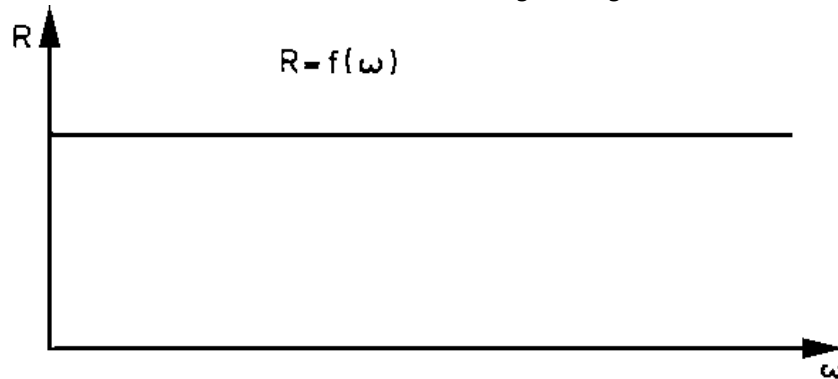


Fig. 7.7. Effective (or active) resistance as a function of frequency

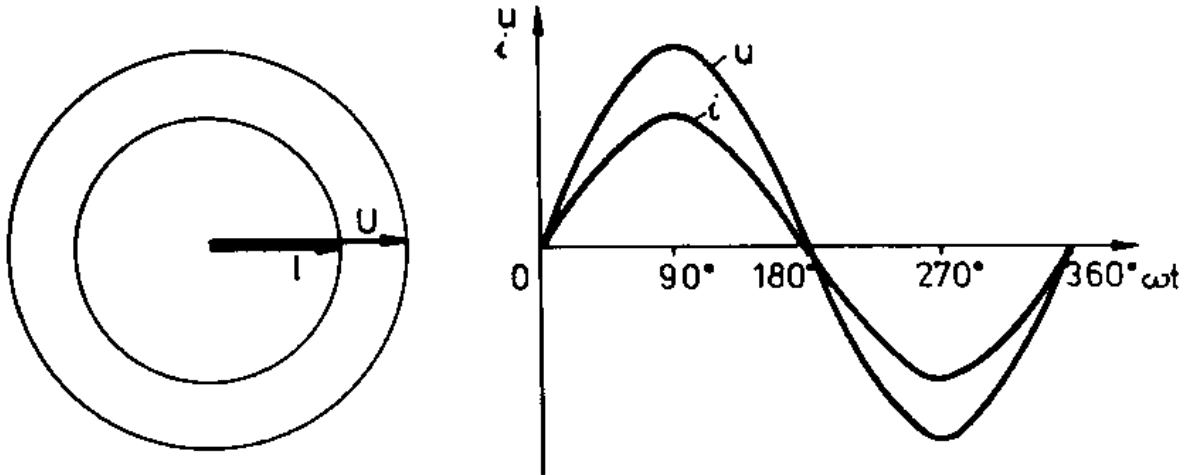


Fig. 7.8. Current and voltage curves for an effective resistance Reactance X

Coils and capacitors do not convert the electrical energy into heat energy but store it in a magnetic or electrical field. Such components have a reactance. A distinction is made between inductive reactances and capacitive reactances.

- **Inductive reactance X_L**

When an alternating current flows through a coil, a voltage is induced in the latter which offers a resistance to the passage of current. This capability of offering resistance is the greater, the greater the inductance and the rate of current variation (hence, the frequency) are. Consequently, the coil has a resistance which increases with increasing frequency.

$$X_L = \omega L = 2\pi fL$$

(7.7.)

where

X_L inductive reactance

ω angular frequency

f frequency

L inductance

$$[X_L] = 1/s \cdot (V \cdot s) / A = V / A = \Omega$$

Fig. 7.9. shows the function $X_L = f(\omega)$

In Section 5.3.3. proof has been given of the fact that a coil imparts sluggishness to a current. When the current passes through its maximum value (for alternating current

this is $\frac{1}{4}$ $\hat{=}$ 90° , its rate of variation has the smallest value and the counter-voltage induced in the coil or the voltage drop is equal to zero. Consequently, there is a

phase shift produced between current and voltage of $90^\circ \hat{=}$ $\frac{\pi}{2}$, that is to say, the current lags behind the voltage. Fig. 7.10. shows vector and line diagrams to illustrate these correlations. Ideal coils do not have an effective resistance and no capacity.

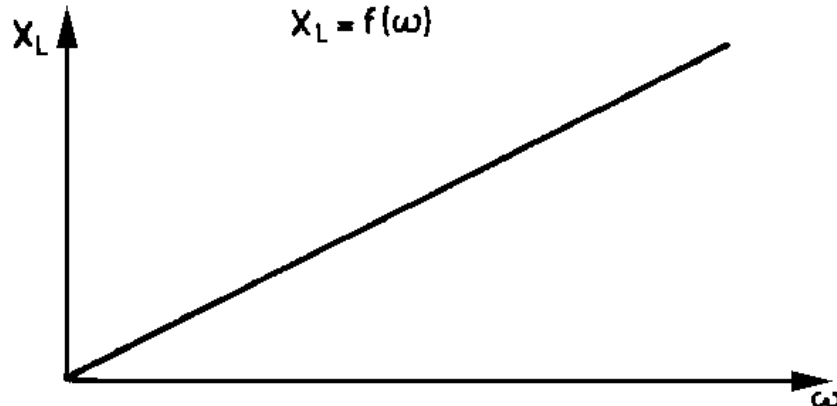


Fig. 7.9. Inductive reactance as a function of frequency

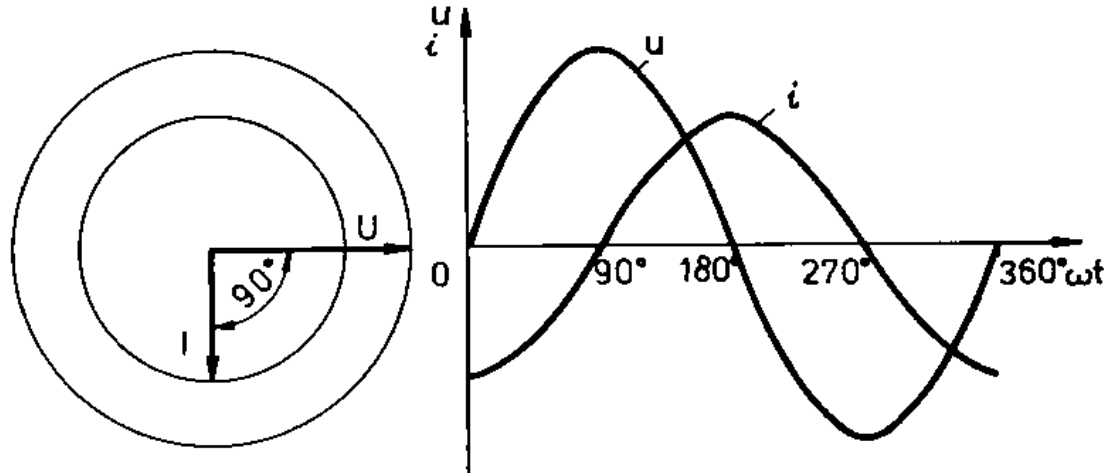


Fig. 7.10. Current and voltage curves for an inductive reactance

Capacitive reactance X_C

When an alternating voltage is applied to a capacitor, then a continuously varying charging and discharging current is produced which apparently penetrates the capacitor. This current is the greater, the greater the capacity and the rate of voltage variation (i.e. the frequency) are. Consequently, the capacitor has a resistance which becomes smaller with increasing frequency.

$$X_C = 1/(\omega C) = 1/(2\pi fC)$$

(7.8.)**where:**

X_C capacitive reactance

ω angular frequency

f frequency

C capacity

$$[X_C] = \frac{1}{\frac{1}{s} \cdot \frac{A \cdot s}{V}} = \frac{V}{A} = \Omega$$

Fig. 7.11. shows the function $X_C = f(\omega)$

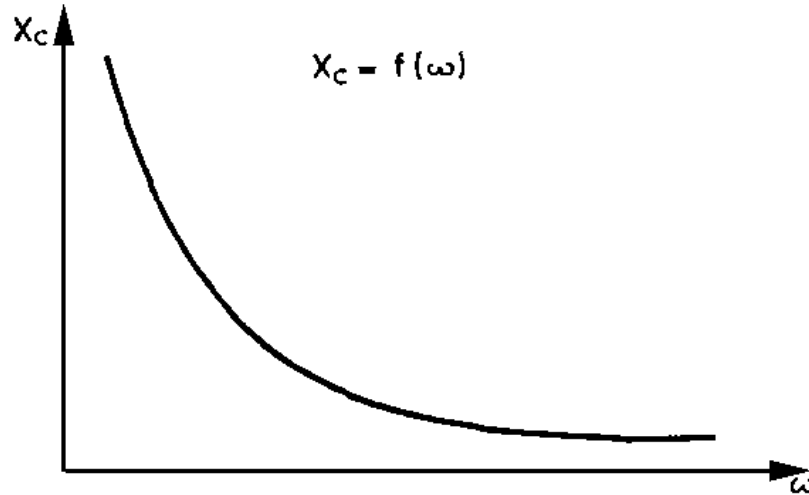


Fig. 7.11. Capacitive reactance as a function of frequency

In Section 6.2.2. it has been explained that no sudden voltage changes are possible in a capacitor. First a current must flow before a voltage can be brought about. Like

in a coil, in this case a phase shift of $90^\circ \triangleq \frac{\pi}{2}$ between voltage and current takes place so that the current is in advance of the voltage.

Fig. 7.12. shows vector diagram and line diagram illustrating these correlations.

Ideal capacitors have no effective resistance and no inductance.

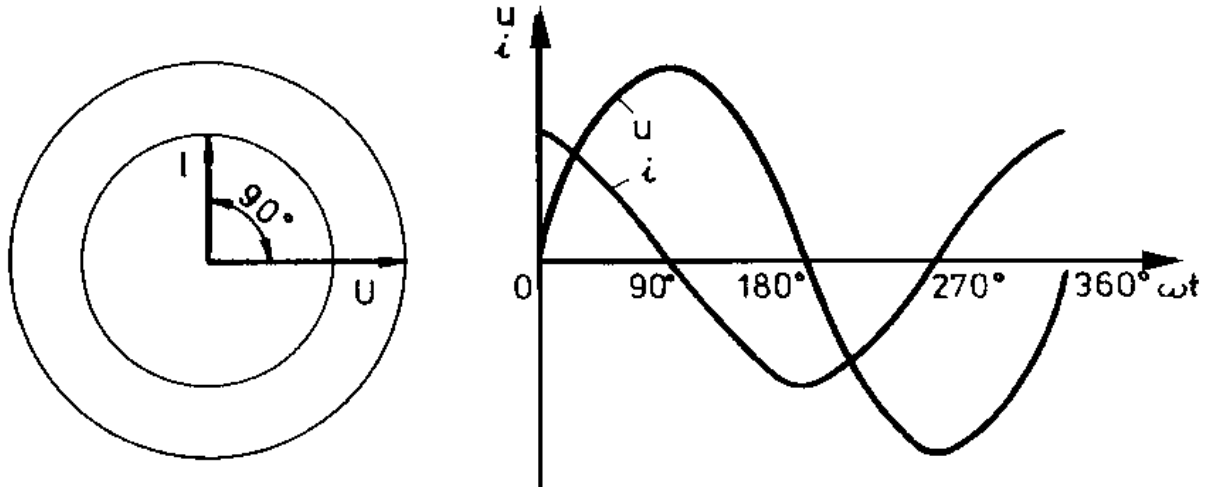


Fig. 7.12. Current and voltage curves for a capacitive reactance Impedance Z

When effective resistances and reactances are connected together, either in series or parallel or series-parallel, then the equivalent resistance of the overall circuit is called impedance Z. It is the quotient of effective voltage value and effective current value.

$$Z = U/I$$

(7.9.)

where:

Z impedance

U effective voltage value

I effective current value

$$[Z] = V/A = \Omega$$

The reciprocal value of the impedance is called, admittance Y:

$$Y = 1/Z$$

Since the phase shift between current and voltage is 0° in effective resistances, 90° in reactances, the following important facts are found:

- An impedance causes a phase shift between current and voltage which is greater than 0° but smaller than 90°

The effective resistances and reactances resulting in the impedance are made up at right angles. This means that, in series connection, Z is always greater than the larger partial resistance but smaller than the algebraic sum of the two. Analogous conditions apply to the admittances in parallel connection.

Written in formular form, we have:

series connection

$$Z = \sqrt{R^2 + X^2}$$

(7.10.)

parallel connection

$$(7.11.)$$

$$\tan \varphi_{\text{series}} = X/R$$

$$(7.12) \quad \tan \varphi_{\text{parallel}} = R/X$$

$$(7.13)$$

$$\varphi(U) = \sqrt{R^2 + (X_L - X_C)^2} \quad (7.12.) \quad \varphi(U) = \sqrt{R^2 + (X_L - X_C)^2} \quad (7.13.)$$

$$\frac{1}{X} = \sqrt{\frac{1}{R^2} + \frac{1}{(X_L - X_C)^2}}$$

If, besides effective resistances, inductive and capacitive reactances are contained in a circuit, attention must be paid to the fact that the phase-shifting effect of the coil (I lags) behind U) is opposed to the action of a capacitor (I is in advance of U). Consequently, these two effects are partly neutralised or, in a special case, fully neutralised. The latter case is called resonance.

In a series connection of L and C, we have for X

$X = |X_L - X_C|$ If $X_L > X_C$, then X is inductive

$X_L < X_C$, then X is capacitive

$X_L = X_C$, then $X = 0$ (resonance)

In case of resonance, the highest current is flowing; it is only limited, by the effective resistance (current increase).

In a parallel connection of L and C, we have for X

$$\frac{1}{X} = \left| \frac{1}{X_L} - \frac{1}{X_C} \right|$$

$X = \left| \frac{1}{(1/X_L - 1/X_C)} \right|$ If $X_L > X_C$ then X is capacitive

$X_L < X_C$ then X is inductive

$X_L = X_C$ then $X \rightarrow \infty$ (resonance)

In case of resonance, the smallest current is flowing, namely, only the current through an effective resistance connected in parallel. When current is supplied at a constant rate, a maximum voltage drop is brought about (voltage increase).

Example 7.3.

A coil with an inductance $L = 200 \text{ mH}$ is connected in series with an effective resistance $R = 100 \Omega$. A current of 500 mA with a frequency of 50 Hz is flowing through the circuit (Fig. 7.13.).

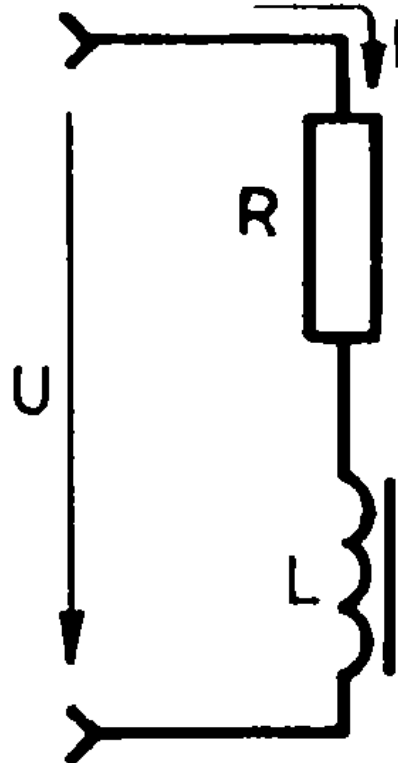


Fig. 7.13 Circuit for example 7.3

Draw the vector diagram for current and voltage true to scale. Calculate the partial voltages, the total voltage and the phase angle between current and voltage!

Given:

$$L = 0.2 \text{ H}$$

$$R = 100 \ \Omega$$

$$I = 0.5 \text{ A}$$

$$f = 50 \text{ Hz}$$

To be found:

vector diagram

U_R ; U_L ; U

φ (u)

Solution:

$$U_R = R I = 100 \ \Omega \cdot 0.5 \text{ A}$$

$$\underline{U_R = 50 \text{ V}}$$

$$U_L = X_L I$$

$$X_L = \omega L = 2\pi f L = 2 \cdot 3.14 \cdot 50 \text{ 1/s} \cdot 0.2 \text{ H}$$

$$X_L = 62.8 \ \Omega$$

$$U_L = 62.8 \ \Omega \cdot 0.5 \text{ A}$$

$$\underline{U_L = 31.4 \text{ V}}$$

Now, the vector diagram can be drawn with the data obtained. The total voltage U 60 V and the phase angle $\varphi = 32^\circ$ are indicated by the length of the vectors.

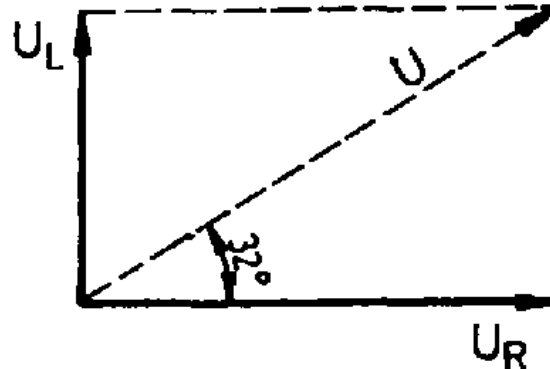


Fig. 7.14. Vector diagram for example 7.5.

Calculation:

$$\mathbf{U} = \mathbf{Z} \cdot \mathbf{I}$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{10,000 + 3,944} \Omega = \sqrt{13,944} \Omega$$

$$\mathbf{Z} = 118 \Omega$$

$$\mathbf{U} = 118 \Omega \cdot 0.5 \text{ A}$$

$$\mathbf{U} = 59 \text{ V}$$

Proof:

$$U = \sqrt{U_R^2 + U_L^2} = 59 \text{ V}$$

$$\tan \varphi = X_L / R$$

$$\tan \varphi = 62.8 / 100 = 0.628$$

$$\varphi = 32^\circ$$

Example 7.4.

A capacitor with a capacity of $C = 5 \text{ nF}$ is connected, in parallel to an effective resistance $R = 100 \text{ k}\Omega$. A voltage of 10 V having a frequency of 300 Hz is applied to the circuit (Fig. 7.15.).

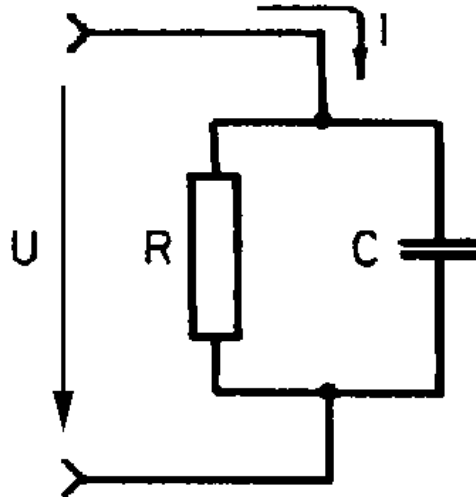


Fig. 7.15. Circuit for example 7.4.

Draw the vector diagram for current and voltage true to scale. Calculate the partial currents, the total current and phase angle between current and voltage!

Given:

$$C = 5 \text{ nF}$$

$$R = 100 \text{ k}\Omega$$

$$U = 10 \text{ V}$$

$$f = 300 \text{ Hz}$$

To be found:

vector diagram

I_R ; I_C ; I

φ (i)

Solution:

$$I_R = U/R = 10 \text{ V}/100 \text{ K}\Omega$$

$$I_R = 100 \text{ }\mu\text{A}$$

$$I_C = U/X_C$$

$$X_C = 1/(\omega C) = 1/(2\pi f C) = 1/(2 \cdot 3.14 \cdot 300 \text{ 1/s} \cdot 5 \cdot 10^{-9} \text{ F})$$

$$X_C = 106 \text{ K}\Omega$$

$$I_C = 10 \text{ V}/106 \text{ k}\Omega$$

$$\underline{I_C = 94 \text{ }\mu\text{A}}$$

Now, the vector diagram can be drawn on the basis of the values obtained above.

The total current $I \approx 140 \mu\text{A}$ and the phase angle of $\varphi 45^\circ$ are indicated by the lengths of the vectors.

Calculation:

$$I = \sqrt{I_R^2 + I_C^2} = \sqrt{10,000 + 8,836} \mu\text{A}$$

$$\underline{\mathbf{I = 137 \mu\text{A}}}$$

Proof:

$$\mathbf{I = U/Z}$$


$$Z = \frac{1}{\sqrt{\frac{1}{R^2} + \frac{1}{X^2}}} = 73 \text{ k}\Omega$$

$$\mathbf{I = 10 \text{ V}/73 \text{ k}\Omega = 137 \mu\text{A}}$$

$$\mathbf{\tan \varphi = R/X_C}$$

$$\mathbf{\tan \varphi = 100/106 = 0.943}$$

$$\mathbf{\varphi = 43^\circ}$$

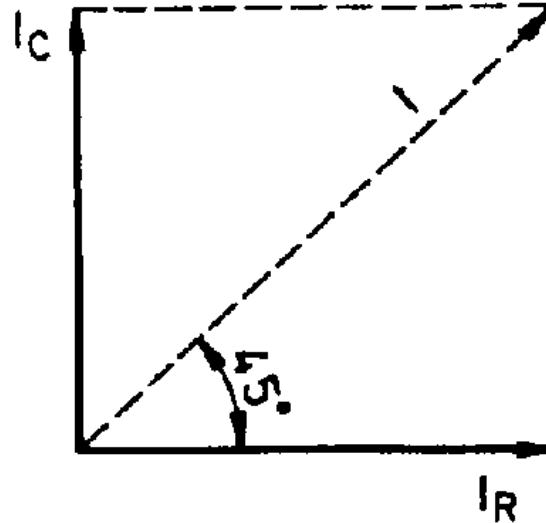

Example 7.5. Vector diagram for example 7.4.

An alternating voltage of 500 mV is applied to a series connection of $R = 250 \Omega$, $L = 200 \mu\text{H}$ and $C = 125 \text{ pF}$. Calculate the maximum possible current and the frequency f_r at which this current will flow!

Given:

$$R = 250 \Omega$$

$$L = 200 \mu\text{H}$$

$$C = 125 \text{ pF}$$

$$U = 500 \text{ mV}$$

To be found: **I_{\max}** **f_r (resonance frequency)****Solution:**

$I_{\max} = U/R$ (case of resonance)

$I_{\max} = 0.5 \text{ V}/250 \Omega = 2 \text{ mA}$

$I_{\max} = 2 \text{ mA}$

resonance at $X_L = X_C$

$X_L = 2\pi fL$

$X_C = 1/(2\pi fC)$

$2 \cdot r_f L = 1/(2\pi f_r C)$

Inversion for results in

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$f_r^2 = 1/(2^2 \pi^2 LC)$$

$$f_r = \frac{1}{2 \cdot 3.14 \sqrt{200 \cdot 10^{-6} \frac{Vs}{A} \cdot 125 \cdot 10^{-12} \frac{As}{V}}}$$

$$f_r = \frac{10^9}{2 \cdot 314 \sqrt{25,000}} \text{ Hz} = \frac{10^9}{2 \cdot 314 \cdot 158} \text{ Hz} = \frac{1000 \cdot 10^6}{992} \text{ Hz} = 1.01 \text{ MHz}$$

$f_r \approx 1 \text{ MHz}$

There are effective resistance, reactances and impedances in the form of loads.

Effective resistance convert the electrical energy completely into heat energy; They are independent of frequency and do not cause phase shifts between current and voltage.

Storage elements such as coils and capacitors have a reactance. It is frequency dependent and causes a 90 ° phase shift between current and voltage. There are inductive and capacitive reactances.

In inductive reactances, the current lags behind the voltage, and in capacitive reactances, the current is in advance of the voltage.

Impedances are interconnections of effective resistances and reactances. They are dependent on frequency because of the reactance included in the system. The magnitude of the impedance can be found by diagrams or by calculation by geometric addition. Depending on the preponderance of the

inductive component or the capacitive component, either the voltage is ahead of the current or vice versa. The phase angle is always between 0° and 90° . If, in one circuit, inductive and capacitive components are present, they neutralise each other partly or completely. The special case where the inductive reactance is equal to the capacitive reactance is called resonance. The frequency in the presence of which resonance occurs is called resonant frequency or frequency of resonance. When resonance is present, a circuit has the behaviour of an effective resistance.

Questions and problems:

- 1. What is the essence of effective (or active) resistances, reactances and impedances?**
- 2. A coil has a reactance of 100Ω at a frequency of 50 Hz. What is the size of the inductance?**
- 3. Represent graphically the curve of the reactance in dependence of the frequency from 0 to 10 kHz for a coil having an inductance of 5 H.**
- 4. At a frequency of 50 Hz, a capacitor has an impedance of about 65Ω . What is the size of its capacity?**
- 5. Represent graphically the curve of the impedance in dependence of the frequency from 0 to 10 kHz for a capacitor with a capacity of $100 \mu\text{F}$!**
- 6. A coil with a loss resistance (effective resistance) of 12Ω connected in series has an impedance of $Z = 20 \Omega$ at a frequency of 50 Hz. The phase angle**

is 53°. Determine the magnitude of the inductive reactance and the inductance by graph and by calculation!

7. What is the frequency f which resonance occurs in a circuit?

7.4. Power of Alternating Current

When loads carry current, a voltage drop is caused. The product of the instantaneous values of current and voltage is called instantaneous power. Normally, the instantaneous power changing from time to time is of less interest than its mean value.

In an effective resistance, current and voltage are in phase. The electrical power becomes completely, i.e. effectively, utilisable. It is called effective power P_e (active power). It can be determined on the basis of the effective values according to the relations derived in Section 4.1.

$$[P_e] = W \text{ (watt)}$$

In a reactance (ideal coil, ideal capacitor), current and voltage are subjected to a phase shift of 90°. The electrical power is required for the duration of a quarter of a cycle for the building up of the magnetic field (in a coil) or of the electrical field (in a capacitor) and delivered in the subsequent quarter of a cycle. There is no power conversion in a temporal mean. This power is called reactive power P_r .

$$[P_r] = \text{Var (voltampere - reactive)}$$

In an impedance, the phase shift between current and voltage is between 0° and 90°.

The electrical power is converted partly as effective power and partly as reactive power. This power is called apparent power P_a .

$$[P_a] = VA \text{ (voltampere)}$$

Since effective resistances and reactances are made up at right angles, this analogously applies to the powers. Consequently, effective and reactive powers are the legs and the apparent power is the hypotenuse of a right-angled triangle having the phase angle (Fig. 7.17.).

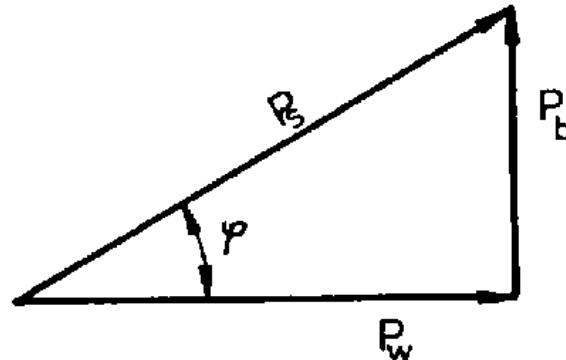


Fig. 7.17. Correlation between effective power, reactive power and apparent power

$$P_w = P_e, P_b = P_r, P_s = P_a$$

From this follows

$$P_a = U \cdot I$$

(7.14)**where:**

Pa apparent power

U effective value of voltage

I effective value of current

From Fig. 7.17. we can derive

$$P_a = \sqrt{P_e^2 + P_r^2}$$

(7.15.)

$$P_e = P_a \cos \varphi$$

(7.16.a)

$$P_r = P_a \sin \varphi$$

(7.16.b)**The expression \cos in equation (7.16.a) is called power factor.**

From equation (7.16.a) we have

$$\cos \varphi = P_e/P_a$$

(7.16.c)

The power factor \cos can be between 0 and 1;

$$0 \leq \cos \varphi \leq 1$$

With a low power factor, the reactive power is high. Since reactive power unnecessarily loads the generators of the power stations and the distribution network, the reactive power must be kept as small as possible for economical reasons; in other words, $\cos \varphi$ must be as high as possible. A power factor of $\cos \varphi = 1$ is an ideal case.

In networks of power electrical engineering, an inductive phase shift occurs always because of the necessary transformers and connected motors; this phase shift always worsens the power factor.

The power factor can be improved up to the value of $\cos \varphi = 1$ by means of an additional capacitive component. In practice, capacitors are connected in parallel having a total capacity of

$$C = P_r/(\omega \cdot U^2)$$

(7.17.)**where**

C capacity required to attain a $\cos \varphi = 1$

P_r reactive power

ω angular frequency

U alternating voltage (effective value)

Of the energy or work has to be determined., then the product of power times time must be formed according to Section 4.1. In accordance with the various types of power, there are effective work, reactive work and apparent work.

Example 7.6.

An enterprise is connected to a 380 V network (50 Hz). A current of 66 A passes through the loads with a power factor of $\cos \varphi = 0.5$. Determine the apparent power, effective power and reactive power and the capacity of the capacitor necessary to improve the power factor to $\cos \varphi = 1$!

Given:

$$\mathbf{U = 380\ V}$$

$$\mathbf{I = 66\ A}$$

$$\mathbf{f = 50\ Hz}$$

$$\mathbf{\cos \varphi = 0.5}$$

To be found:

P_a , P_e , P_r , C

Solution:

$$P_a = U I$$

$$P_a = 380 \text{ V} \cdot 66 \text{ A} = 25,000 \text{ VA}$$

$$\underline{P_a = 25 \text{ kVA}}$$

$$P_e = P_a \cos \varphi$$

$$P_e = 25 \text{ kVA} \cdot 0.5$$

$$\underline{P_e = 12.5 \text{ kW}}$$

$$P_r = P_a \sin \varphi$$

$$\sin \varphi = \sqrt{1 - \cos^2 \varphi} = \sqrt{1 - 0.25} = 0.865$$

$$P_r = 25 \text{ kVA} \cdot 0.865$$

$$\underline{P_r = 21.6 \text{ kVar}}$$

Proof with equation (7.15.)

$$P_a = \sqrt{P_e^2 + P_r^2}$$

$$P_a = \sqrt{154 + 469} \text{ kVA} = \sqrt{635} \text{ kVA} = 25 \text{ kVA}$$

$$C = P_r / (\omega U^2)$$

$$C = \frac{21,600V \cdot A}{2 \cdot 3.14 \cdot 50 \frac{1}{s} \cdot 380^2 V^2} \approx 476 \mu F$$

$$\underline{C \approx 500 \mu F}$$

With a capacitor connected in parallel with the loads having a capacity of C 500 μF , the bad power factor of $\cos \varphi = 0.5$ can be increased to the ideal value of $\cos \varphi = 1$.

With alternating current, there are three types of powers, namely, apparent power, effective power and reactive power. Effective power and reactive power are made up at right angles. The apparent power is always greater than effective power or reactive power but it is always smaller than the algebraic sum of the latter two. Efforts are always made to achieve a high effective power and a reactive power which is as small as possible. The ratio of effective power to apparent power is called power factor. It can reach the value of 1 in the most favourable case. The power factor can be improved when a capacitor is connected in parallel with the loads.

Questions and Problems:

- 1. What are the differences between effective power, reactive power and apparent power?**
- 2. What are the values of the effective power and reactive power when the apparent power is 23 kVA with a phase angle of $\varphi = 30^\circ$?**

3. Why is a high power factor desired in energy supply systems? Explain measures by means of which the power can be improved!

4. Two motors are connected, in parallel and to a supply system of 220 V. One motor has a power factor of 0.65 and carries a current of 2 A; the other motor having a power factor of 0.85 carries a current of 5.5 A. Calculate for the total circuit the effective power, reactive power and apparent power and the total power factor!

