

Signals & Variables (3A)

Simulation & Synthesis

Copyright (c) 2012 Young W. Lim.


Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.


This document was produced by using OpenOffice and Octave.

Sequential Assignment (1)

 
```
process (A)
  signal S: std_logic ;
begin
  S <= not A ;
  Y <= not S ;
end process;
```



 
```
process (A)
  signal S: std_logic ;
begin
  S <= not A ; after 3 ns;
  Y <= not S ; after 1 ns;
end process;
```


 
```
process (A)
  signal S: std_logic ;
begin
  Y <= not S ;
  S <= not A ;
end process;
```



 
```
process (A)
  signal S: std_logic ;
begin
  Y <= not S ; after 1 ns;
  S <= not A ; after 3 ns;
end process;
```






Sequential Assignment (1)

 
```
process (A)
  signal S: std_logic ;
begin
  S <= A after 3 ns;
  Y <= S after 1 ns;
end process;
```


   
```
process (A)
  signal S: std_logic ;
begin
  Y <= S after 1 ns;
  S <= A after 3 ns;
end process;
```




Sequential Assignment (1)

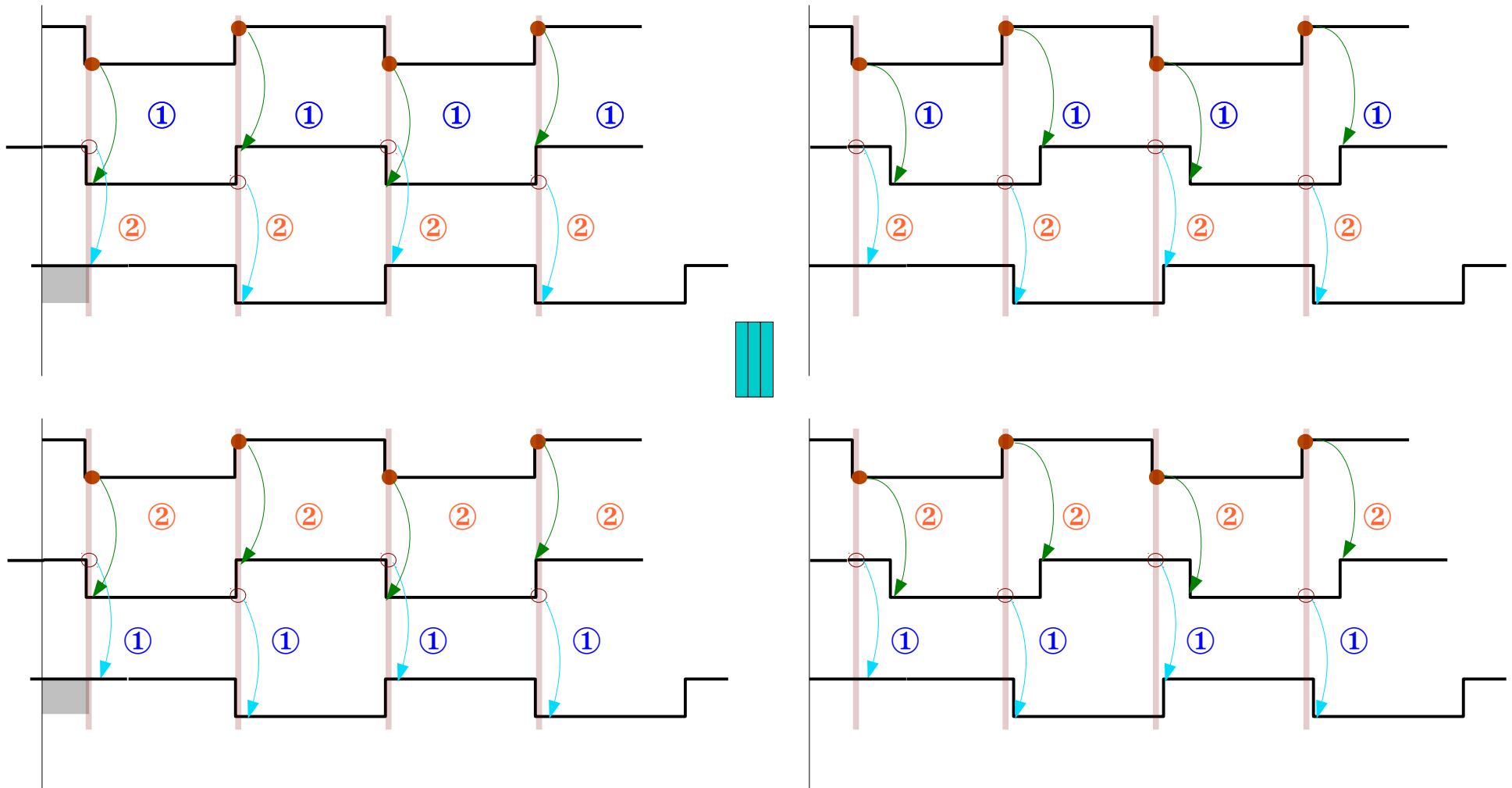


Sequential Assignment (2)

 
```
process (A, S)
  signal S: std_logic ;
begin
  S <= not A ;
  Y <= not S ;
end process;
```



 
```
process (A, S)
  signal S: std_logic ;
begin
  S <= not A ; after 3 ns;
  Y <= not S ; after 1 ns;
end process;
```


 
```
process (A, S)
  signal S: std_logic ;
begin
  Y <= not S ;
  S <= not A ;
end process;
```



 
```
process (A, S)
  signal S: std_logic ;
begin
  Y <= not S ; after 1 ns;
  S <= not A ; after 3 ns;
end process;
```




Sequential Assignment (2)

 
```
process (A, S)
  signal S: std_logic ;
begin
  S <= not A ;
  Y <= not S ;
end process;
```



 
```
process (A, S)
  signal S: std_logic ;
begin
  S <= not A ; after 3 ns;
  Y <= not S ; after 1 ns;
end process;
```


 
```
process (A, S)
  signal S: std_logic ;
begin
  Y <= not S ;
  S <= not A ;
end process;
```



 
```
process (A, S)
  signal S: std_logic ;
begin
  Y <= not S ; after 1 ns;
  S <= not A ; after 3 ns;
end process;
```




Sequential Assignment (2)

 
```
process (A, S)
  signal S: std_logic ;
begin
  S <= not A ;
  Y <= not S ;
end process;
```



 
```
process (A, S)
  signal S: std_logic ;
begin
  S <= not A ; after 3 ns;
  Y <= not S ; after 1 ns;
end process;
```


 
```
process (A, S)
  signal S: std_logic ;
begin
  Y <= not S ;
  S <= not A ;
end process;
```




```
process (A, S)
  signal S: std_logic ;
begin
  Y <= not S ; after 1 ns;
  S <= not A ; after 3 ns;
end process;
```

 


Ex 1
 
```
process (A, B, C)
  variable M: std_logic ;
begin
  M := A or B ;
  Y <= M or C after 1 ns;
end process;
```



```
process (A, B, C)
  variable M: std_logic ;
begin
  Y <= M or C after 1 ns;
  M := A or B ;
end process;
```

 


Ex 2

```
process (A, B, C, M)
  signal M: std_logic ;
begin
  M <= A or B ; after 3 ns;
  Y <= M or C ; after 1 ns;
end process;
```

```
process (A, B, C, M)
  signal M: std_logic ;
begin
  Y <= M or C ; after 1 ns;
  M <= A or B ; after 3 ns;
end process;
```


Ex 3

```
process (Clock)
  variable M: std_logic ;
begin
  if rising_edge(Clock) then
    M := A or B ;
    Y <= M or C after 1 ns;
  end if;
end process;
```

 


Ex 4

```
process (Clock)
  signal M: std_logic ;
begin
  if rising_edge(Clock) then
    M | <= A or B ; | after 3 ns;
    Y | <= M or C | after 1 ns;
  end if;
end process;
```

 

Ex 4

```
process (Clock)
  signal M: std_logic ;
begin
  if rising_edge(Clock) then
    M | <= | A or B ; | after 3 ns;
    Y | <= | M or C | after 1 ns;
  end if;
end process;
```

 

Variable & FlipFlop (1)

```
process (Clock)
  variable M, N: std_logic
begin
  if rising_edge(Clock) then
    Y <= N;
    N := M;
    M := X;
  end if;
end process;
```

```
process (Clock)
  variable M, N: std_logic
begin
  if rising_edge(Clock) then
    M := X;
    N := M;
    Y <= N;
  end if;
end process;
```

Variable & FlipFlop (2)

```
process (Clock)
  variable A : std_logic (3 downto 0) ;
begin
  if rising_edge(Clock) then
    for i in 3 downto 0 loop
      A(i) := A(i-1) ;
    end loop
    A(0) := Data ;
    YA := A ;
  end if;
end process;
```

```
process (Clock)
  variable B : std_logic (0 to 3) ;
begin
  if rising_edge(Clock) then
    for i in 0 to 3 loop
      B(i) := B(i-1) ;
    end loop
    B(0) := Data ;
    YB := B ;
  end if;
end process;
```

Variable & FlipFlop (3)

```
process (Clock)
  signal A : std_logic (3 downto 0) ;
begin
  if rising_edge(Clock) then
    for i in 3 downto 0 loop
      A(i)    <=  A(i-1) ;
    end loop
    A(0)     <=  Data ;
    YA      <=  A ;
  end if;
end process;
```

```
process (Clock)
  signal B : std_logic (0 to 3) ;
begin
  if rising_edge(Clock) then
    for i in 0 to 3 loop
      B(i)    <=  B(i-1) ;
    end loop
    B(0)     <=  Data ;
    YB      <=  B ;
  end if;
end process;
```


References

- [1] <http://en.wikipedia.org/>
- [2] J. V. Spiegel, VHDL Tutorial,
http://www.seas.upenn.edu/~ese171/vhdl/vhdl_primer.html
- [3] J. R. Armstrong, F. G. Gray, Structured Logic Design with VHDL
- [4] Z. Navabi, VHDL Analysis and Modeling of Digital Systems
- [5] D. Smith, HDL Chip Design
- [6] <http://www.csee.umbc.edu/portal/help/VHDL/stdpkg.html>
- [7] VHDL Tutorial - VHDL online www.vhdl-online.de/tutorial/