

Signals & Variables (3A)

Simulation & Synthesis

Copyright (c) 2012 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.


This document was produced by using OpenOffice and Octave.

Sequential Assignment (1)

```
process (A)
```

```
    signal S: std_logic ;
```

```
begin
```

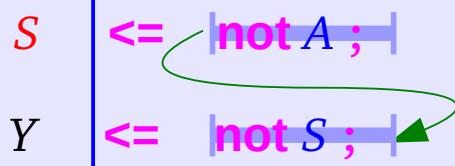


```
end process;
```

```
process (A)
```

```
    signal S: std_logic ;
```

```
begin
```

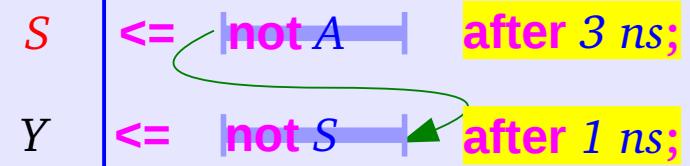


```
end process;
```

```
process (A)
```

```
    signal S: std_logic ;
```

```
begin
```

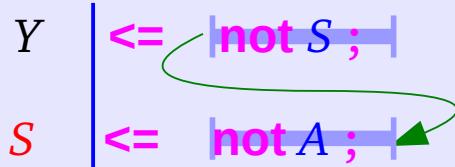


```
end process;
```

```
process (A)
```

```
    signal S: std_logic ;
```

```
begin
```

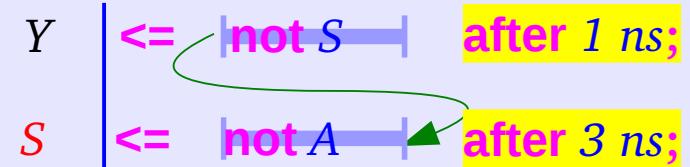


```
end process;
```

Sequential Assignment (2)

```
process (A, S)
```

```
    signal S: std_logic ;
```

```
begin
```

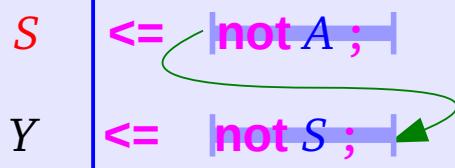


```
end process;
```

```
process (A, S)
```

```
    signal S: std_logic ;
```

```
begin
```

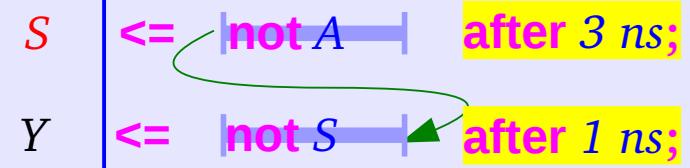


```
end process;
```

```
process (A, S)
```

```
    signal S: std_logic ;
```

```
begin
```

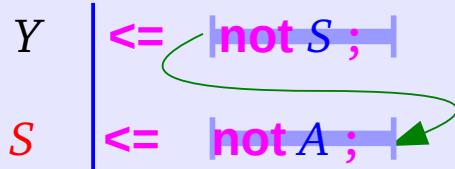


```
end process;
```

```
process (A, S)
```

```
    signal S: std_logic ;
```

```
begin
```

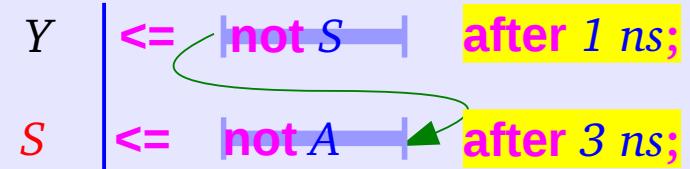

```
end process;
```

Ex 1

```
process (A, B, C)
    variable M: std_logic ;
begin
    M := A or B ;
    Y <= M or C after 1 ns;
end process;
```

```
process (A, B, C)
    variable M: std_logic ;
begin
    Y <= M or C after 1 ns;
    M := A or B ;
end process;
```

Ex 2

```
process (A, B, C, M)
    signal M: std_logic ;
begin
    M |<=| A or B ; after 3 ns;
    Y |<=| M or C ; after 1 ns;
end process;
```

```
process (A, B, C, M)
    signal M: std_logic ;
begin
    Y |<=| M or C ; after 1 ns;
    M |<=| A or B ; after 3 ns;
end process;
```

Ex 3

```
process (Clock)
    variable M: std_logic ;
begin
    if rising_edge(Clock) then
        M := A or B;
        Y <= M or C after 1 ns;
    end if;
end process;
```

Ex 4

```
process (Clock)
    signal M: std_logic ;
begin
    if rising_edge(Clock) then
        M |<=| A or B ; after 3 ns;
        Y |<=| M or C |+| after 1 ns;
    end if;
end process;
```

Ex 4

```
process (Clock)
    signal M: std_logic ;
begin
    if rising_edge(Clock) then
        M |<=| A or B ; after 3 ns;
        Y |<=| M or C |+| after 1 ns;
    end if;
end process;
```

Variable & FlipFlop (1)

```
process (Clock)
    variable M, N: std_logic
begin
    if rising_edge(Clock) then
        Y <= N;
        N := M;
        M := X;
    end if;
end process;
```

```
process (Clock)
    variable M, N: std_logic
begin
    if rising_edge(Clock) then
        M := X;
        N := M;
        Y <= N;
    end if;
end process;
```

Variable & FlipFlop (2)

```
process (Clock)
  variable A : std_logic (3 downto 0) ;
begin
  if rising_edge(Clock) then
    for i in 3 downto 0 loop
      A(i)      :=  A(i-1) ;
    end loop
    A(0)      :=  Data ;
    YA        :=  A ;
  end if;
end process;
```

```
process (Clock)
  variable B : std_logic (0 to 3) ;
begin
  if rising_edge(Clock) then
    for i in 0 to 3 loop
      B(i)      :=  B(i-1) ;
    end loop
    B(0)      :=  Data ;
    YB        :=  B ;
  end if;
end process;
```

Variable & FlipFlop (3)

```
process (Clock)
    signal A : std_logic (3 downto 0) ;
begin
    if rising_edge(Clock) then
        for i in 3 downto 0 loop
            A(i)      <=  A(i-1) ;
        end loop
        A(0)      <=  Data ;
        YA       <=  A ;
    end if;
end process;
```

```
process (Clock)
    signal B : std_logic (0 to 3) ;
begin
    if rising_edge(Clock) then
        for i in 0 to 3 loop
            B(i)      <=  B(i-1) ;
        end loop
        B(0)      <=  Data ;
        YB       <=  B ;
    end if;
end process;
```

References

- [1] <http://en.wikipedia.org/>
- [2] J. V. Spiegel, VHDL Tutorial,
http://www.seas.upenn.edu/~ese171/vhdl/vhdl_primer.html
- [3] J. R. Armstrong, F. G. Gray, Structured Logic Design with VHDL
- [4] Z. Navabi, VHDL Analysis and Modeling of Digital Systems
- [5] D. Smith, HDL Chip Design
- [6] <http://www.csee.umbc.edu/portal/help/VHDL/stdpkg.html>
- [7] VHDL Tutorial - VHDL online www.vhdl-online.de/tutorial/