

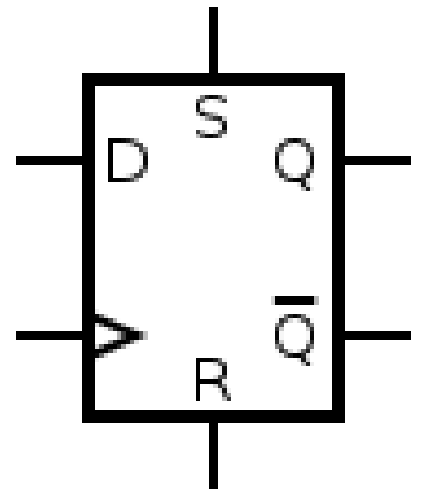


Output Stage Latch

 


Input Stage Latch

 




Output Stage Latch

 


	CLK=0	CLK=0 → 1	CLK= 1
	S=1 R=1	When D=0 S=1 R=0 When D=1 S=0 R=1	When D=0 → 1 S=1 R=0 When D=1 → 0 S=0 R=1
	Maintain output latch	D=0/1 at the rising edge reset / set the output latch	Maintain reset / set at the rising edge regardless of input changes

Input Stage Latch – CLK = 0

 

SR=11


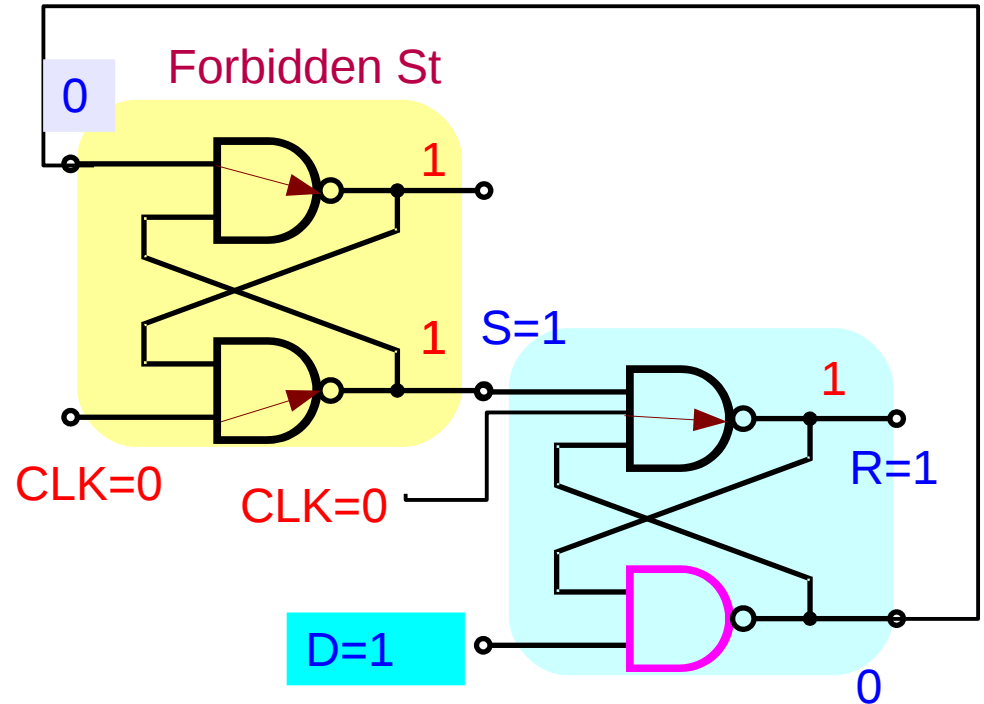


If the clock is low, both the output signals of the input stage are high regardless of the data input; the output latch is unaffected and it stores the previous state.

Input Stage Latch – Rising Edge

$D=0 \rightarrow SR=10$

$D=1 \rightarrow SR=01$

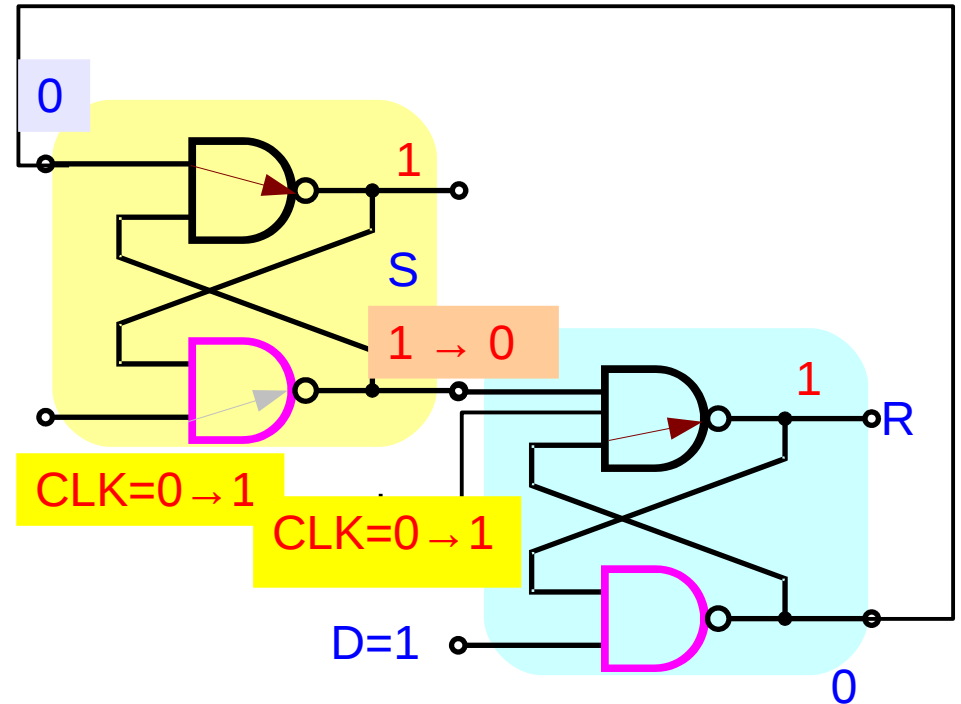 

When the clock signal changes from low to high, (rising edge) only one of the output voltages (S or R) goes low (depending on the data signal D) and sets/resets the output latch:

($D=0 \rightarrow SR = 10 \rightarrow$ reset the output latch $\rightarrow Q= 0$)

($D=1 \rightarrow SR = 01 \rightarrow$ set the output latch $\rightarrow Q = 1$)



if $D = 0$, the lower output becomes low ; (Reset operation $SR=10$)

if $D = 1$, the upper output becomes low. (Set operation $SR=01$)

Input Stage Latch – CLK=1

$D=(0 \rightarrow 1) \rightarrow SR=10$

$D=(1 \rightarrow 0) \rightarrow SR=01$

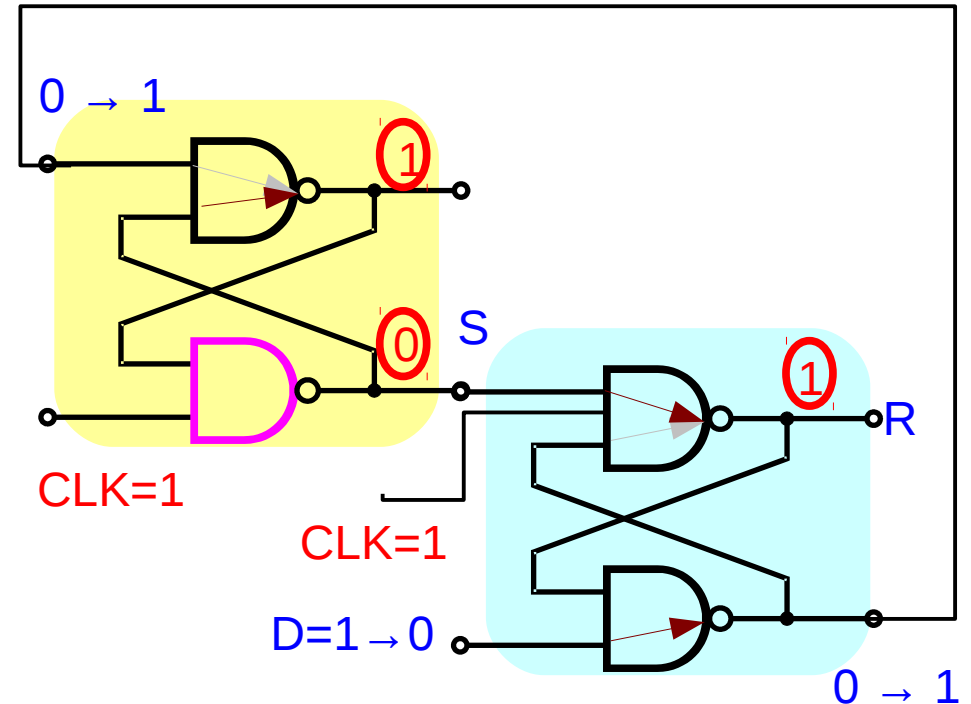 

If the clock signal continues staying **high**, the outputs keep their states regardless of the data input ($D=0$: $SR=10$, $D=1$: $SR=01$ at the rising edge) and force the output latch to stay in the corresponding state as the input logical zero remains active ($SR=10$: Reset, $SR=01$: Set) while the clock is **high**.

The input stage processes the clock and data signals to ensure correct input signals for the output stage.

The circuit is closely related to the gated D latch as both the circuits convert the **two D input states** ($D = 0 / 1$) to **two input combinations** ($SR = 10 / 01$) for the output SR latch by inverting the data input signal (both the circuits split the single D signal in two complementary S and R signals).

The difference is that in the gated D latch, **simple NAND logical gates** are used while in the positive-edge-triggered D flip-flop, **SR NAND latches** are used for this purpose.

The role of these latches is to **"lock"** the active output producing low voltage (a logical zero); thus the positive-edge-triggered D flip-flop can be thought of as **a gated D latch** with **latched input gates**.

SR = 11 is maintained when CLK = 0
→ output remains in its present state

At the rising edge (CLK=0 → 1),
if D=0 then R → 0 : RESET (Q=0)

After the rising edge (CLK=1),
R=0 is maintained even if D changes because Q = 0.

The FF is locked out and
is unresponsive to further changes in the input


At the falling edge (CLK=1 → 0),
R → 1 without changing output (HOLD state)

At the rising edge (CLK=0 → 1),
if D=1 then S → 0 : SET (Q=1)

After the rising edge (CLK=1),
S=0 is maintained even if D changes.

At the falling edge (CLK=1 → 0),
S → 1 without changing output (HOLD state)

NAND RS Latch

 

$S' = 0$
 $R' = 1$

$S' = 1$
 $R' = 0$

$S' = 0$
 $R' = 1$


$S' = 1$
 $R' = 0$

$S' = 1$
 $R' = 1$

$S' = 1$
 $R' = 1$

$S' = 1$
 $R' = 1$

$S' = 1$
 $R' = 1$

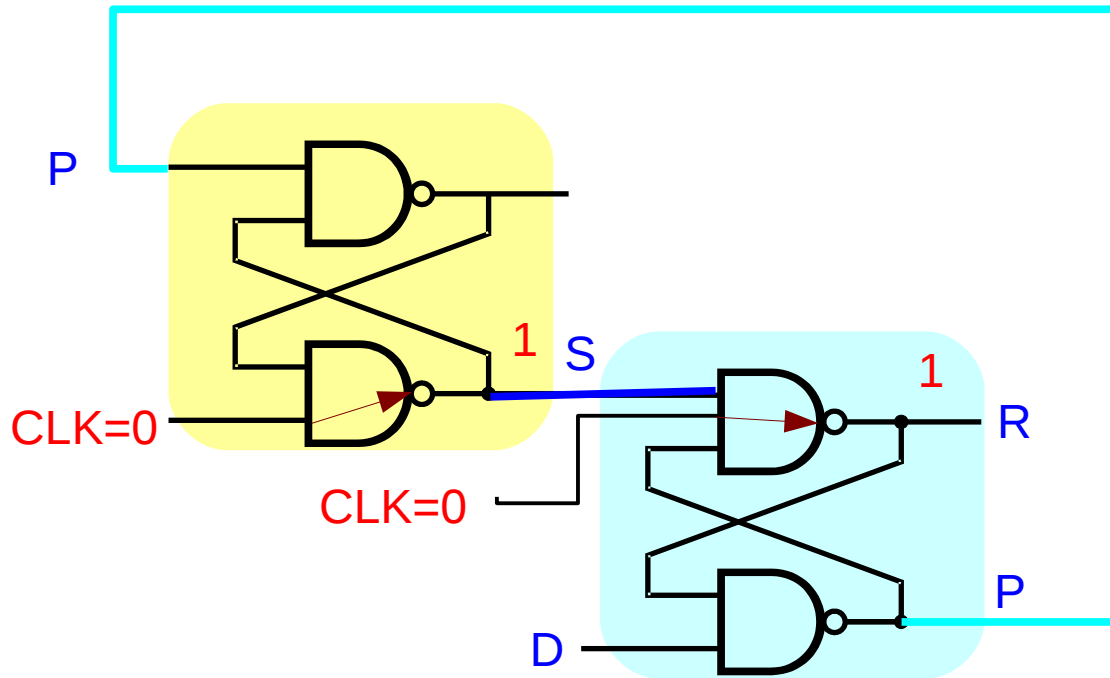

CLK=0

L1 in Reset

L1 in forbidden

if P=0

if P=1

L2 in Set if D=1


S=1, R=1,
P=0

X

L2 in forbidden if D=0

X

S=1, R=1,
P=1

 





CLK=1		L1 in Set if $P=0$	L1 in Hold if $P=1$
L2 in Set	if $S=0, D=1$	$S=0, R=1, P=0$	X
L2 in Reset	if $S=1, D=0$	X	$S=1, R=0, P=1$
L2 in Hold	if $S=1, D=1$	X	$S=1, R=0, P=1$
L2 in Forbidden	if $S=0, D=0$	X	$S=0, R=1, P=1$


SET op for the output latch

When $CLK=1$, regardless of D

$S=0$

$R=1$

 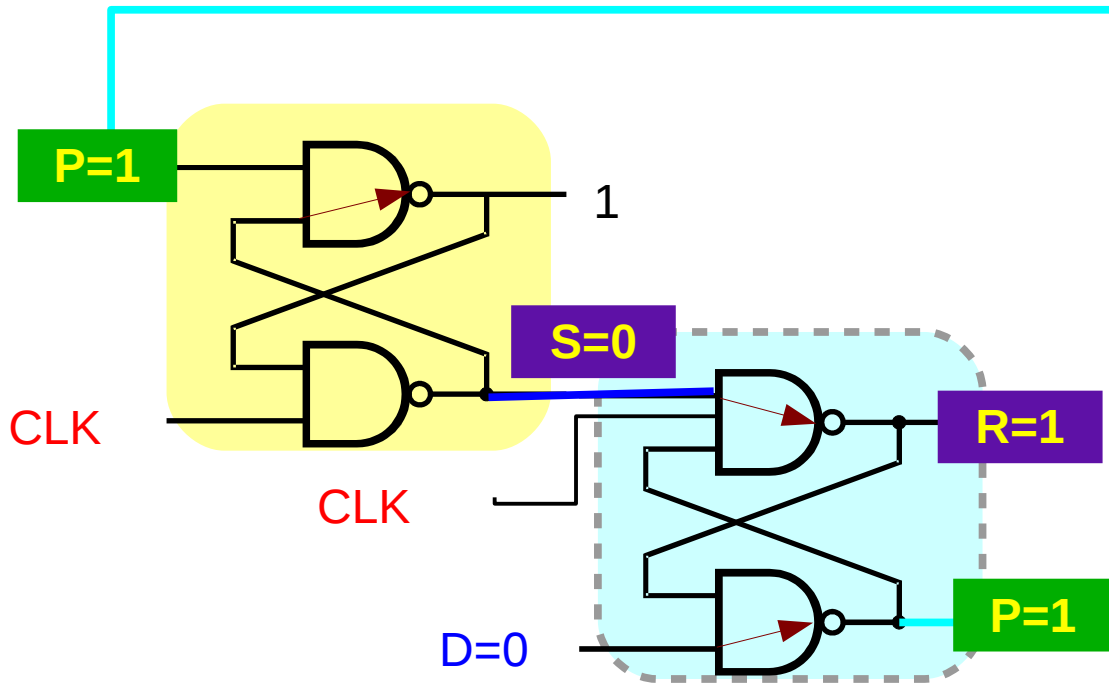 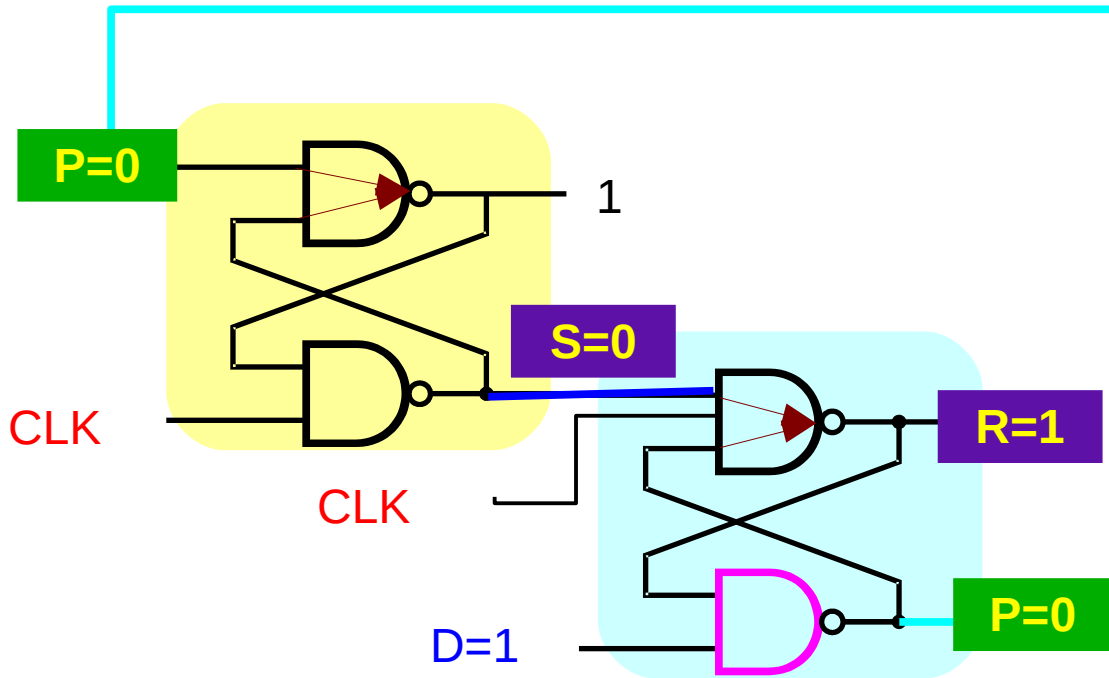

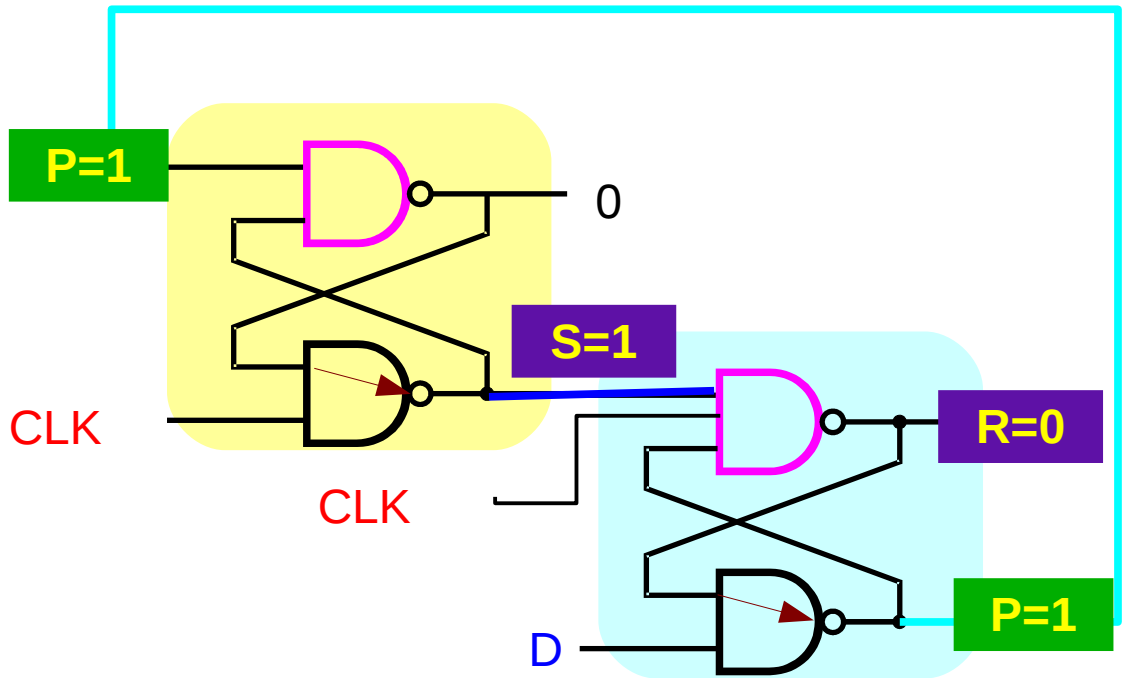

RESET op for the output latch

When **CLK=1**, regardless of **D**


S=1 **R=0**

CLK=0 → ~~F=1~~ → CLK=1
 D=0 / 1


HOLD op for the output latch

When $CLK=0$, regardless of D


S=1 **R=1**

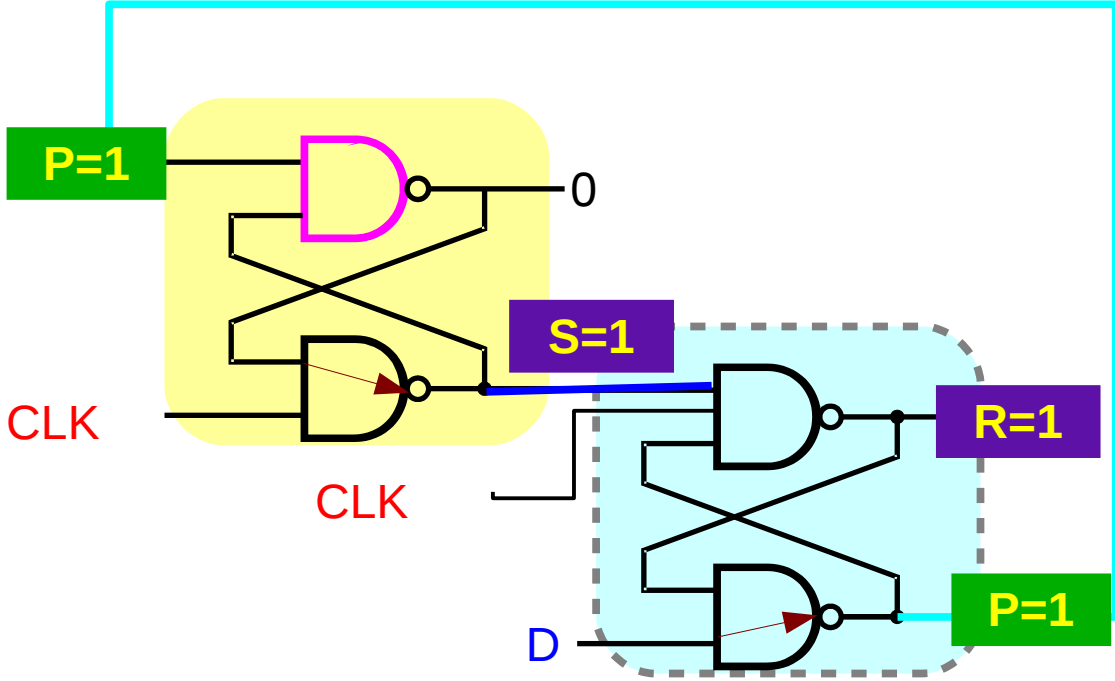

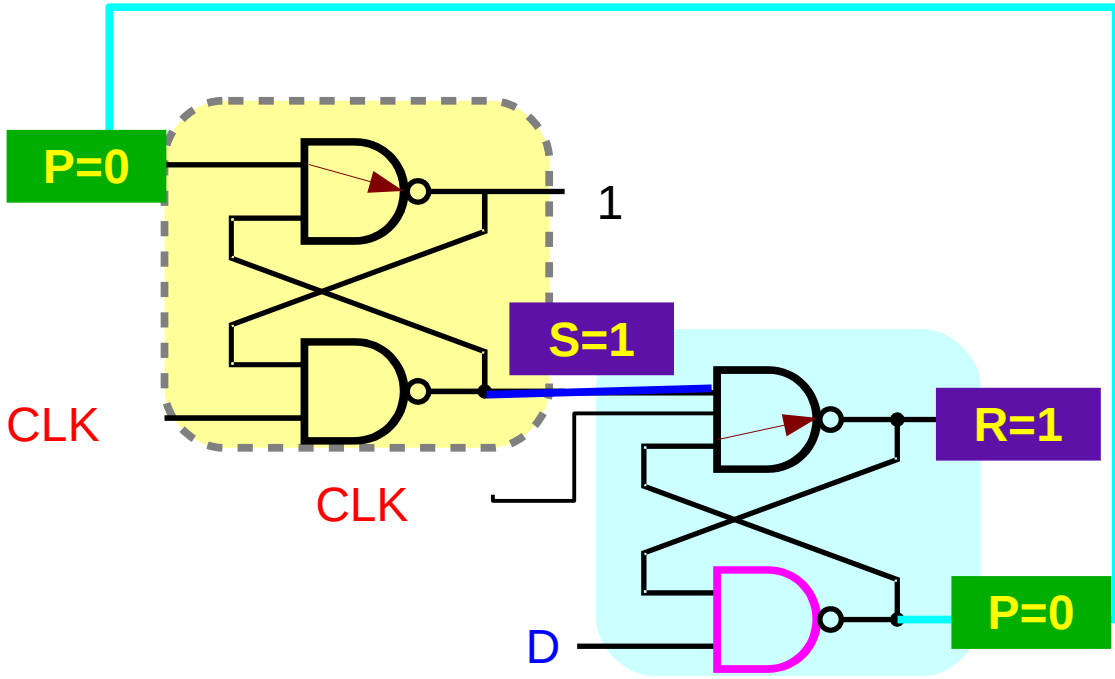$CLK=1 \rightarrow R=0$ $CLK=0$
 $D=0 \rightarrow P=1$



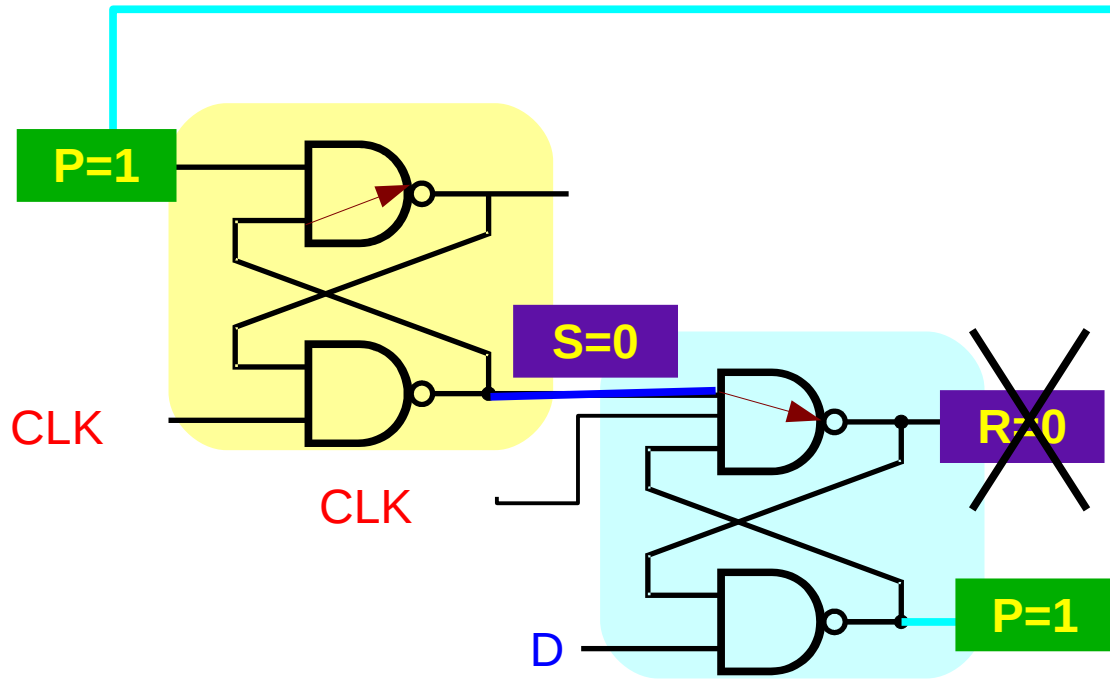$CLK=1 \rightarrow S=0$ $CLK=0$
 $D=1 \rightarrow P=1$



Forbidden for the output latch

Impossible to enter

CLK=0

CLK=1

HOLD op for the output latch

SET, RESET op for the output latch

S=1

R=1


S=0

R=1

S=1

R=0

Output Stage Latch

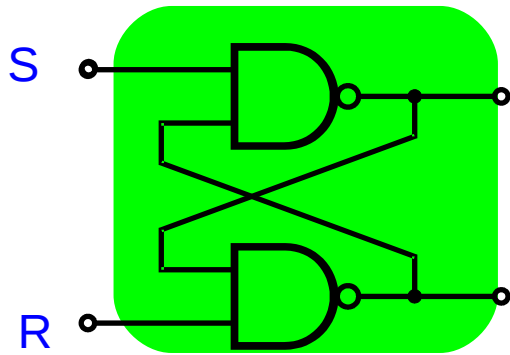

CLK=0 → 1

When D=0
HOLD → RESET

When D=1
HOLD → SET

CLK=1 → 0


RESET → HOLD

SET → HOLD


Rising edge CLK=0→1

HOLD → RESET / SET

If D=0	SR=11	→	SR=10
If D=1	SR=11	→	SR=01

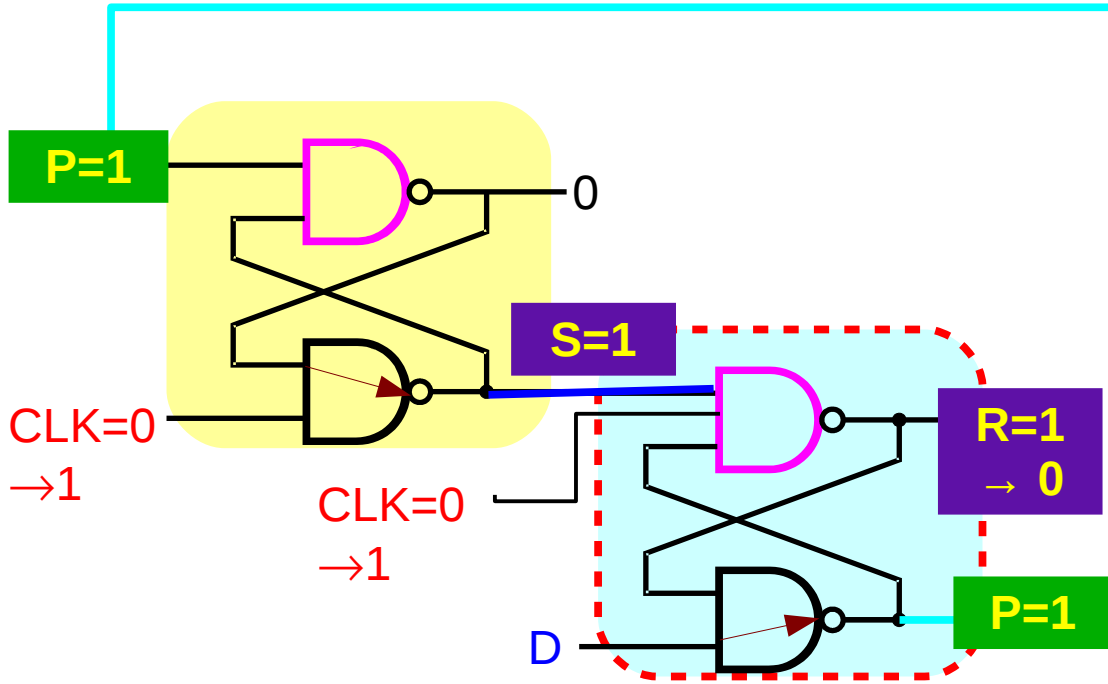

CLK=1 → R=0
D=0 → P=1

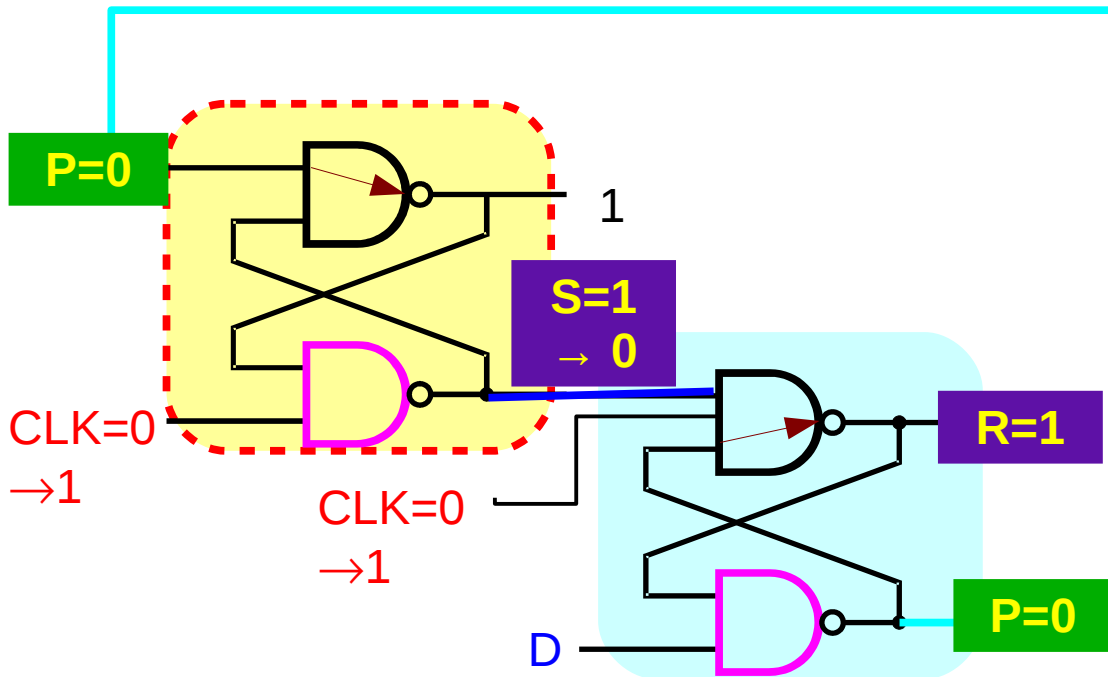

CLK=1 → S=0
D=1 → P=1


Falling edge CLK=1→0

SET → HOLD

SR=01




SR=11

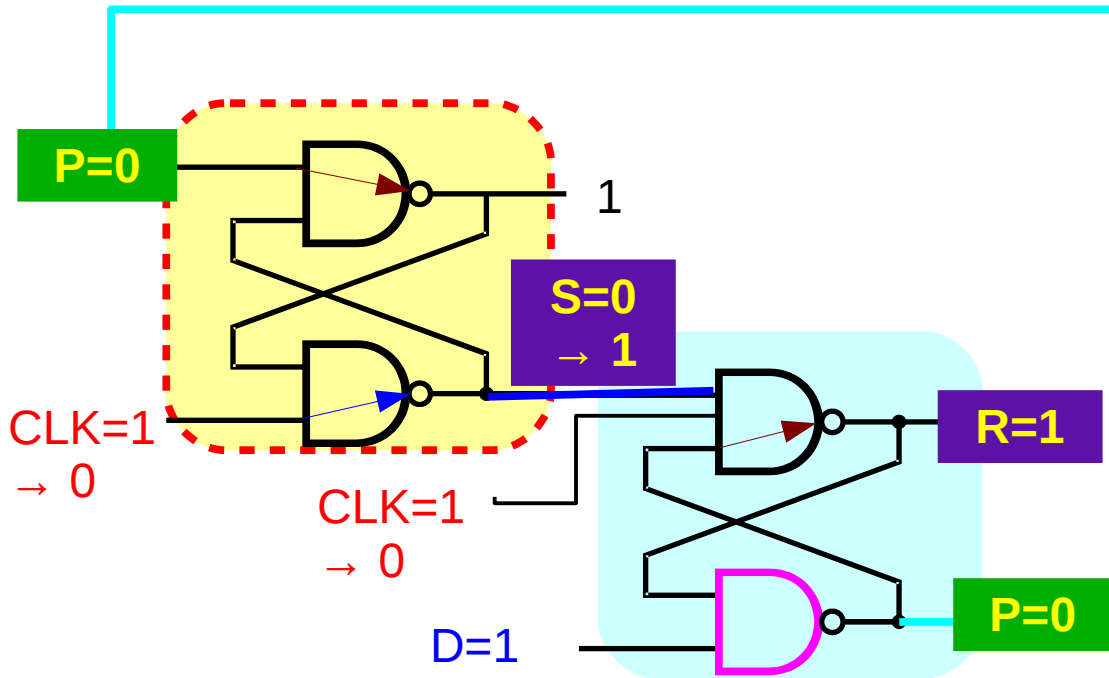

CLK=0 → S=1

D=1 → P=0

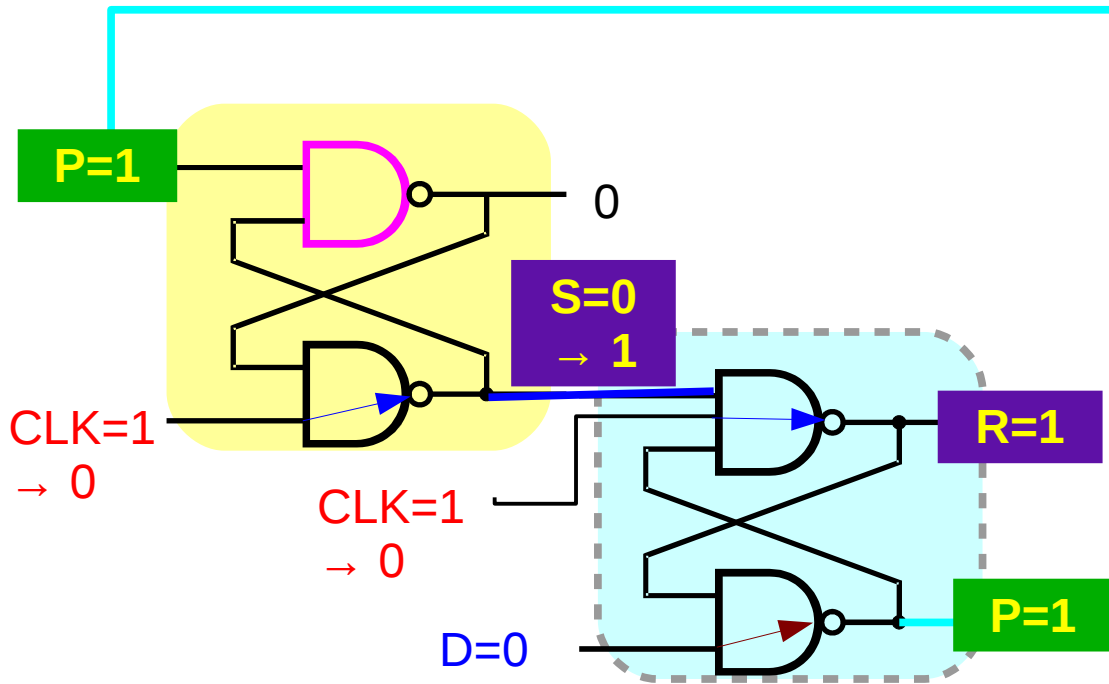

CLK=0 → S=1

D=0 → P=1

